

# Phase noise in SiGe HBT amplifiers and applications

*O. Llopis, S. Gribaldo*

LAAS-CNRS, 7 av. du Colonel Roche, 31077 Toulouse, FRANCE

e-mail : llopis@laas.fr

## Outline :

Amplifier residual phase noise, as a tool to study nonlinear noise in transistors

- ➡ Measurement technique
- ➡ Specificity of the characterization of SiGe devices
- ➡ Residual phase noise modelling of SiGe transistors

Application to the design of a two stages low phase noise SiGe amplifier

Application to the phase noise characterization and modelling of new types of microwave frequency stabilization devices : FBAR resonators and optical resonators

# Introduction : noise in oscillators

*What is the origin of an oscillator short term frequency fluctuation ?*

- 1) phase fluctuations in the active device (amplifier)  
*resulting from the baseband noise  
or directly from the HF noise*



Main problem at microwave frequencies  
where the devices are small and often  
sustain high 1/f noise

- 2) resonator 1/f noise

Not a problem in passive microwave resonators  
but a real problem with piezoelectric resonators


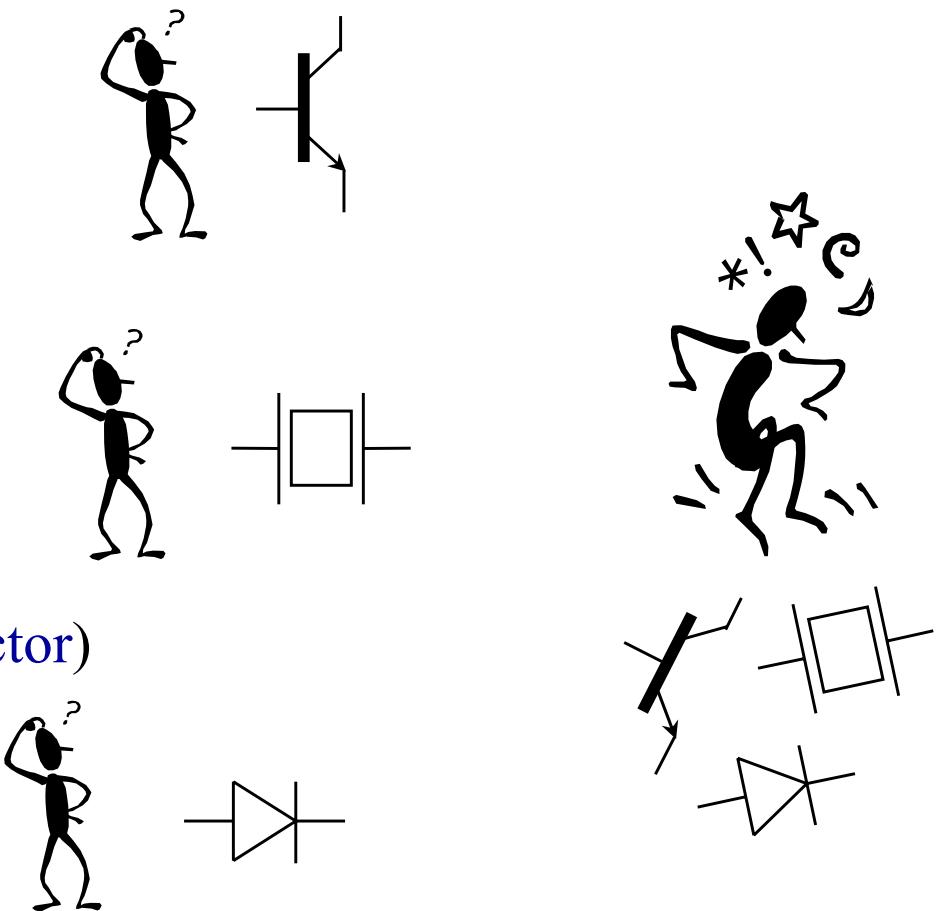
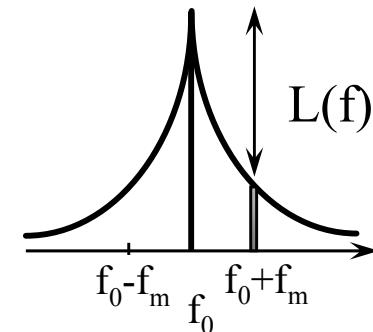
- 3) control element phase noise (ex : varactor)

Not too much studied – not too strong  
Nonlinear noise not related to baseband noise



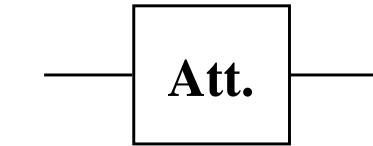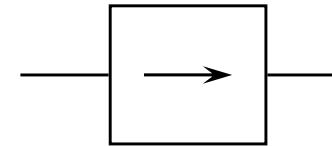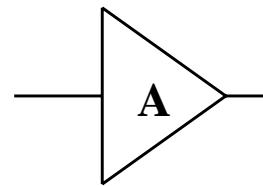
#### 4) output buffer phase noise

May have an influence if active. Should be modelled in the same way as the oscillator active element



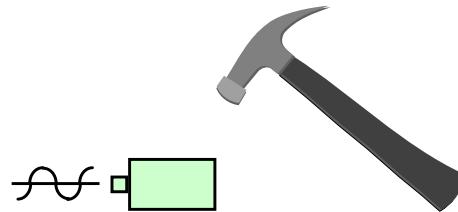
#### 5) sensitivity to an external mechanical perturbation (vibration)




Need of a high quality mechanical embedding
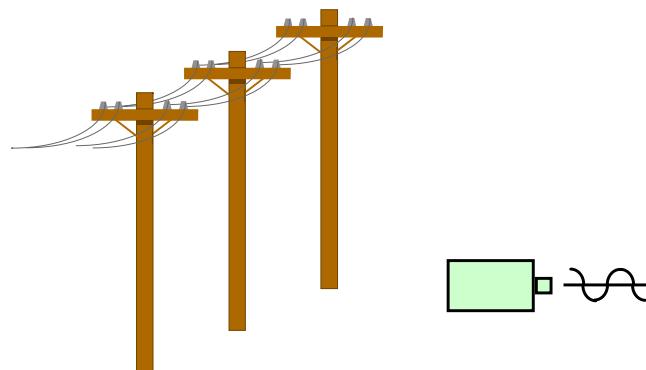
#### 6) sensitivity to an external electrical perturbation



Need of a good electrical shielding
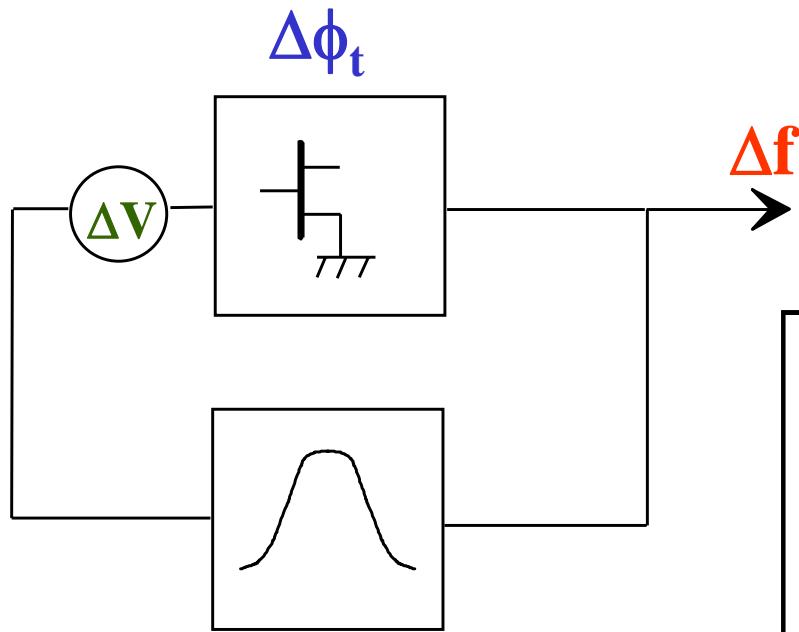
# The simplified feedback oscillator model




$$\frac{d\phi}{df} = \frac{2Q}{f}$$

$$\Delta f = \frac{\Delta\phi_t}{\frac{d\phi}{df}} = \frac{f_0}{2Q} \Delta\phi_t$$

$\Delta f$  = oscillator frequency noise

$\Delta\phi_t$  = transistor (open loop) phase noise

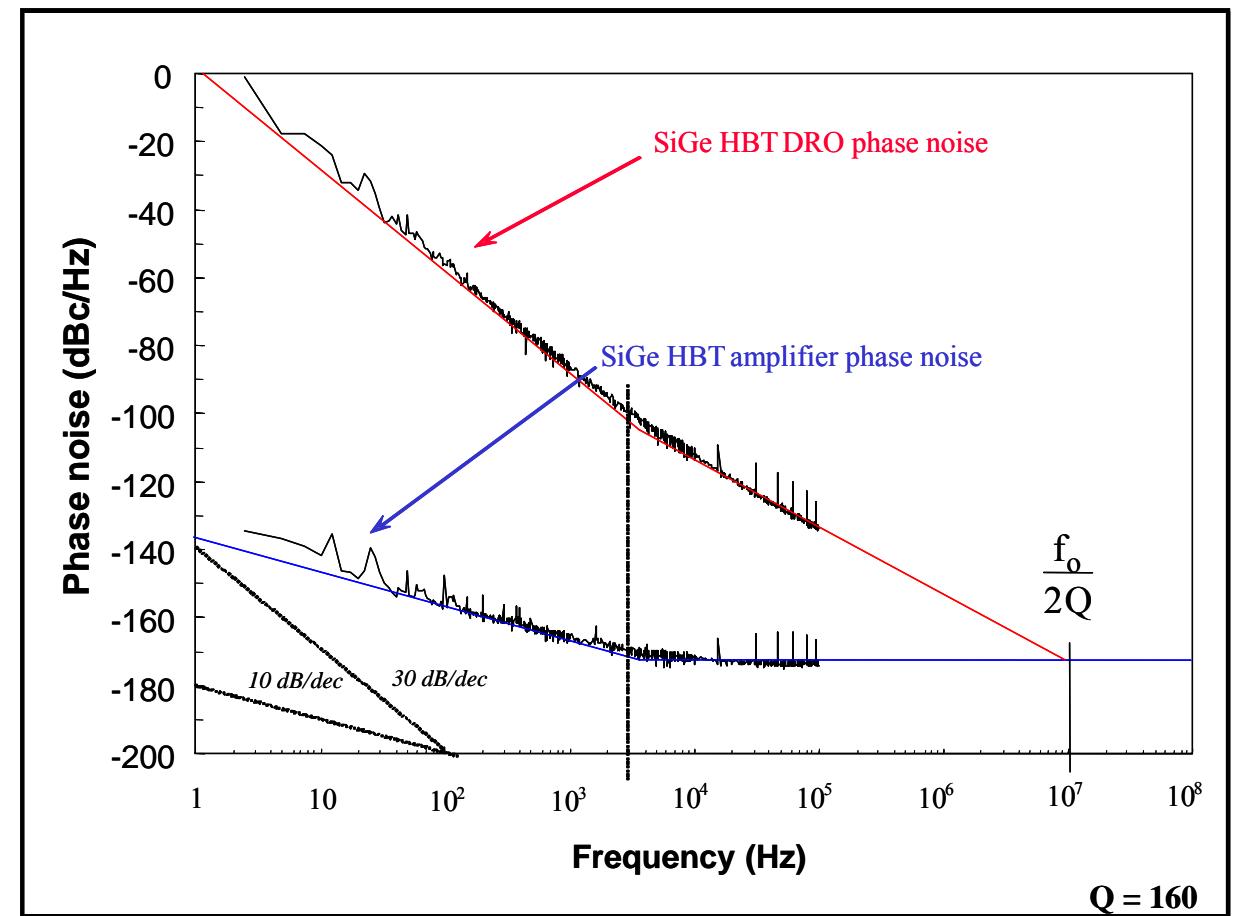$\Delta V$  = equivalent input noise voltage (LF or HF)



Example of phase to frequency conversion in a 4 GHz SiGe HBT oscillator

# Residual phase noise measurement of low phase noise amplifiers and transistors

Advantages of open loop (or residual) phase noise studies versus oscillator phase noise studies :

## SIMULATION


- ➡ Faster for a driven circuit than an autonomous circuit
- ➡ Possibility to analyse the noise conversion both in linear and nonlinear modes

## MEASUREMENT

- ➡ Better control of the parameters (no needs for a loop phase control)
- ➡ Measurement either in linear and nonlinear modes

# Amplifier phase noise characterisation

*Optimised measurement bench*

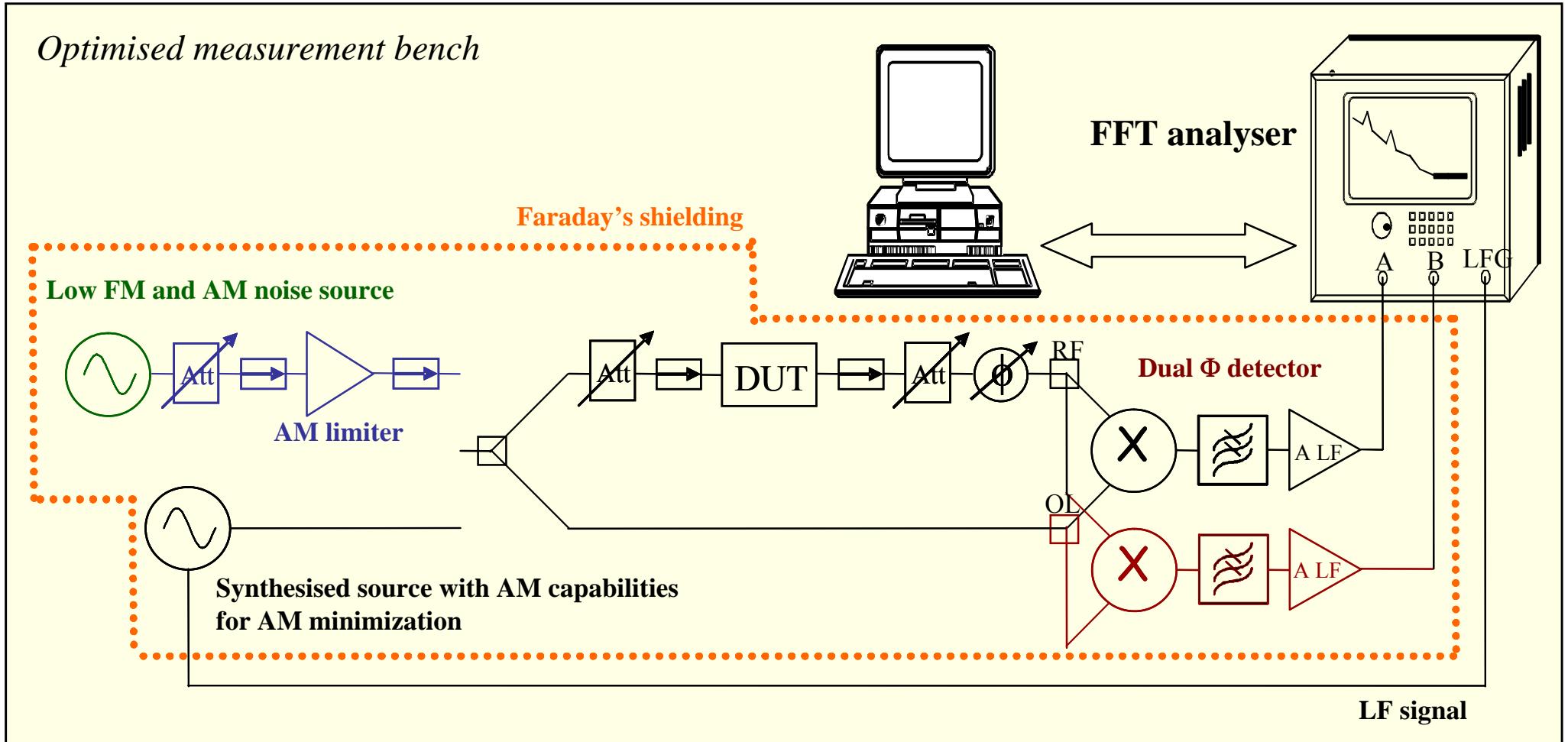


$$\Delta \bar{V}_s^2 = G^2 K_\phi^2 \Delta \bar{\varphi}_t^2 + (2\pi f)^2 G^2 K_\phi^2 \Delta \bar{f}^2 + G^2 K_{AM}^2 \Delta \bar{A}^2 + G^2 K_\phi^2 \Delta \bar{\varphi}_{mel}^2 + G^2 \Delta \bar{V}_{ampli}^2$$


Annotations for the equation:

- DUT noise**: Points to the term  $G^2 K_\phi^2 \Delta \bar{\varphi}_t^2$ .
- Noise Floor**: Points to the term  $G^2 \Delta \bar{V}_{ampli}^2$ .
- Delay balance and low phase noise source**: Points to the term  $(2\pi f)^2 G^2 K_\phi^2 \Delta \bar{f}^2$ .
- AM limiter and low AM noise source**: Points to the term  $G^2 K_{AM}^2 \Delta \bar{A}^2$ .
- Low I/f noise Si detector / amplifier + cross-correlation detection**: Points to the term  $G^2 K_\phi^2 \Delta \bar{\varphi}_{mel}^2$ .

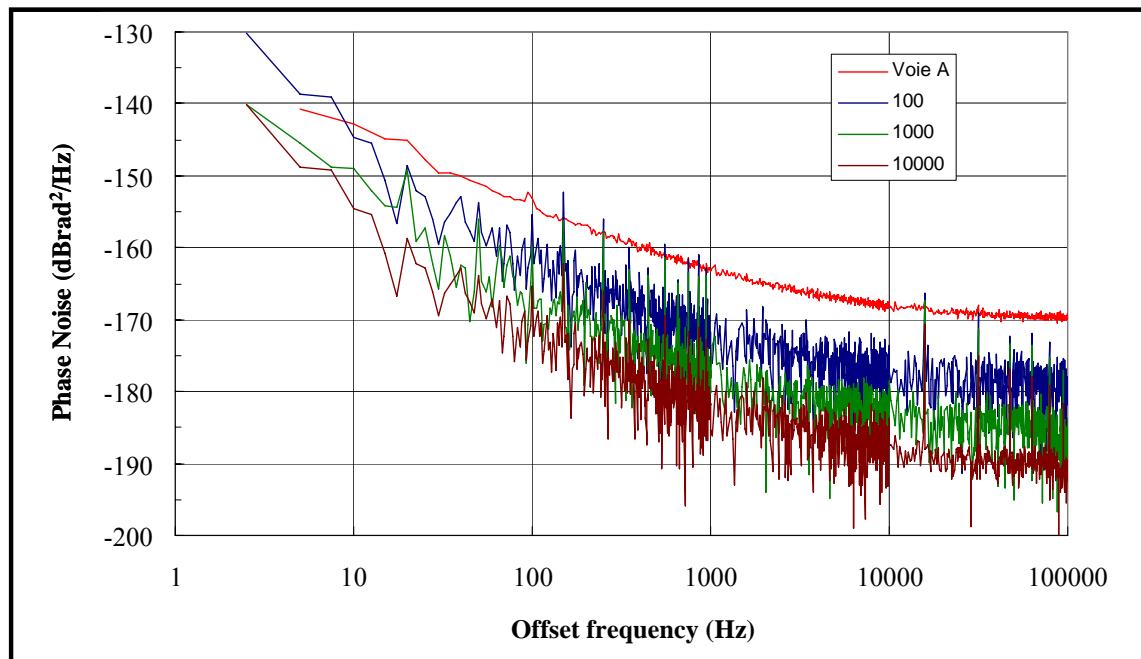
# Amplifier phase noise characterisation : measurement capabilities and AM rejection problem



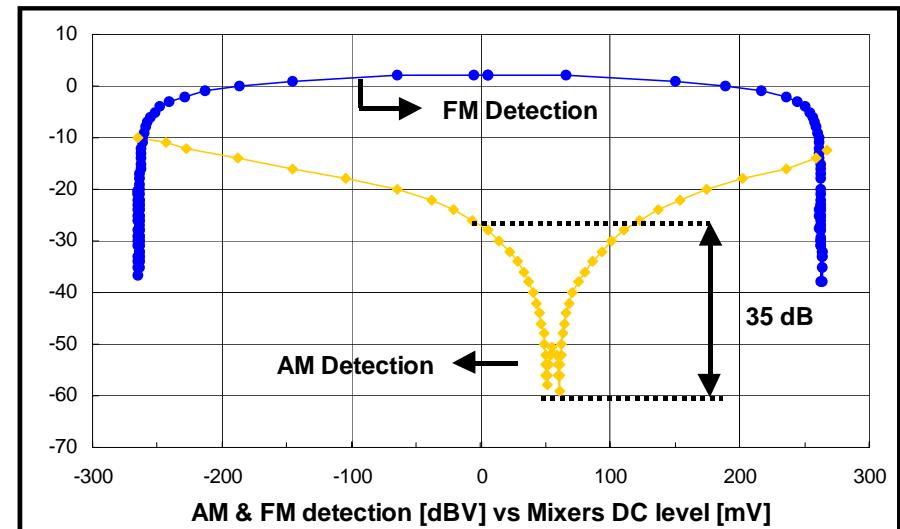*Advantage of the dual detector / cross-spectrum technique : effect of the averaging number on the 3.5 GHz noise floor*



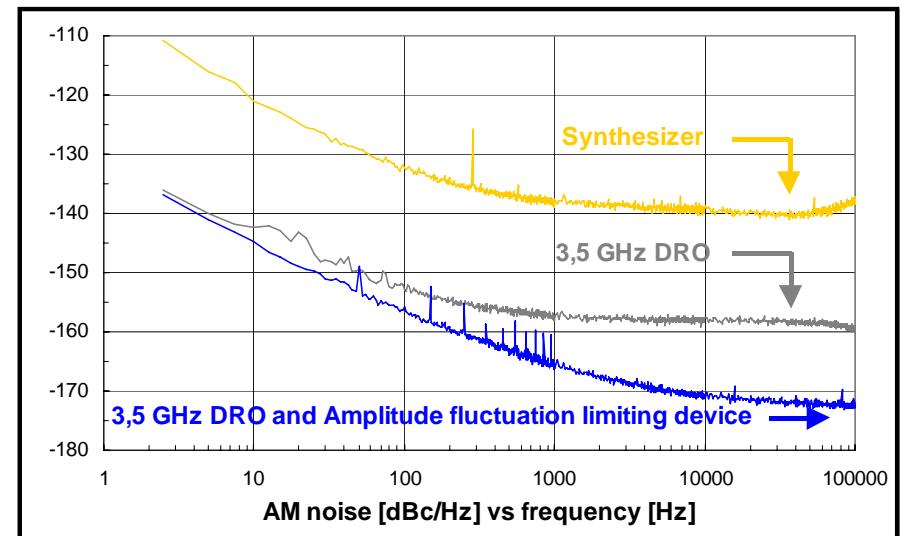
*Phase (or frequency) detection, at the mixer level versus mixer DC output*



G. Cibiel et al., IEEE Trans. on UFFC, jan. 2004

*AM noise of different microwave sources*
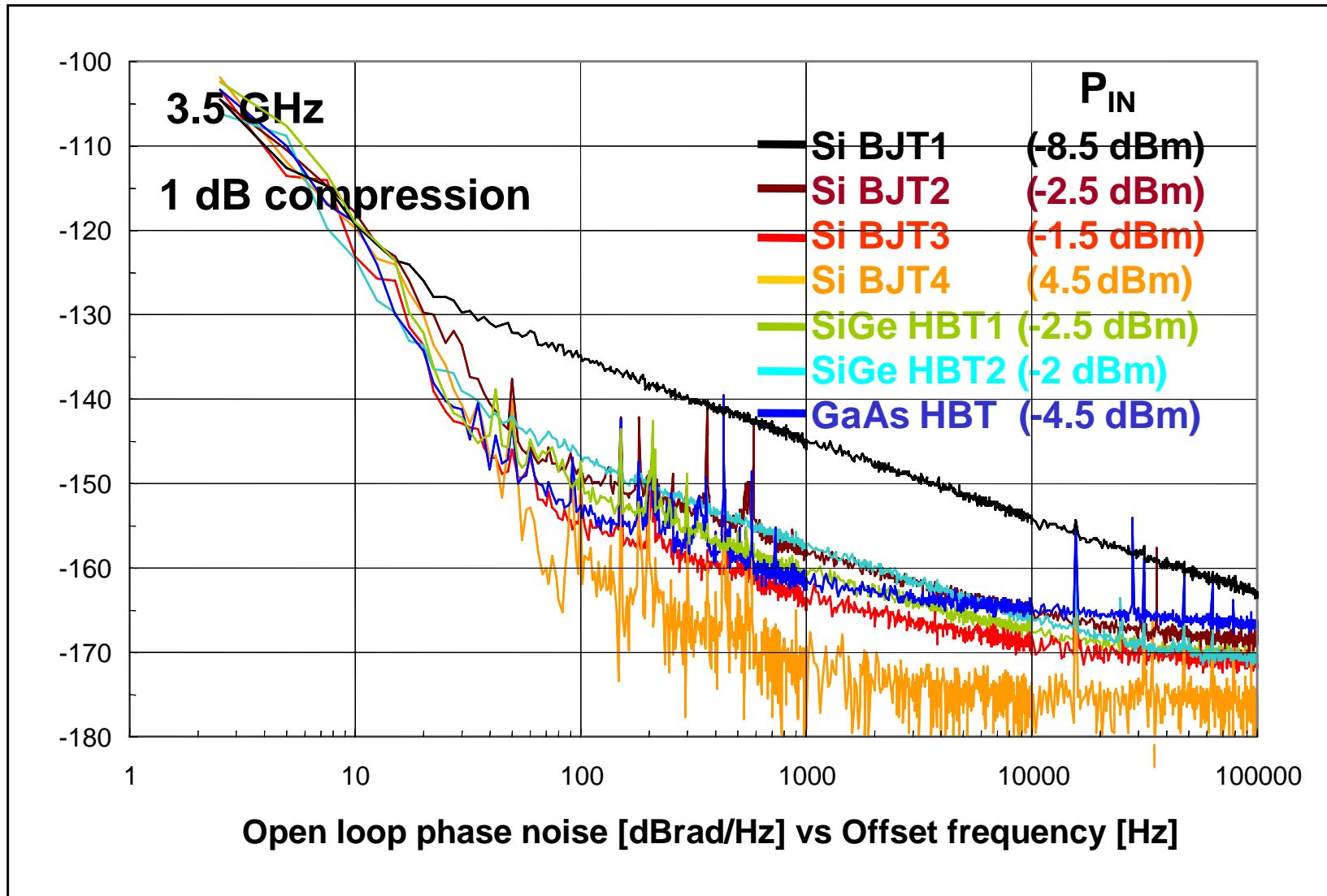
## Phase noise in microwave transistors : *device selection for low phase noise oscillator design*




In this experiment, the devices are maintained onto  $50 \Omega$  load at RF (3.5 GHz), using two isolators, and are battery biased with a low impedance bias on the collector and a capacitive filtering of the LF current noise  $Si_{be}$  on the base bias (low impedance above 100 Hz)

G. Cibiel et al., 2003 GAAS Symp.
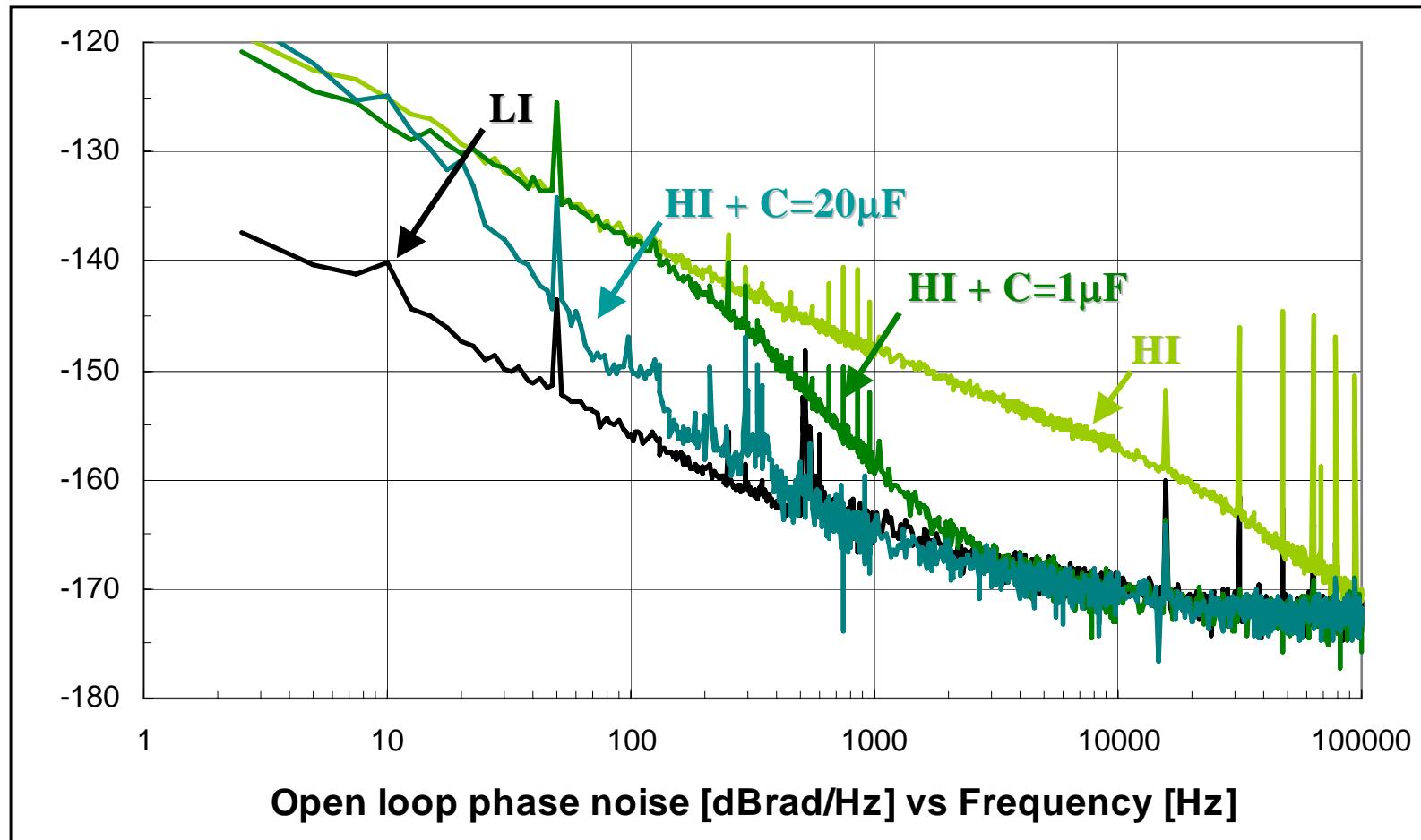
# Phase noise in microwave SiGe HBTs :

*investigations on the effect of the base bias network on the phase noise of a SiGe HBT*




**Residual phase noise of an SiGe HBT amplifier at 3.5 GHz (LPNT 32, SiGe Semiconductor)**  
 Three types of base bias networks are compared : high impedance bridge, capacitive filtering and low impedance

**The low impedance bias cancels the effect of the Si<sub>be</sub> low frequency noise source**


*G. Cibiel et al., IEEE Trans. on UFFC, jan. 2004*
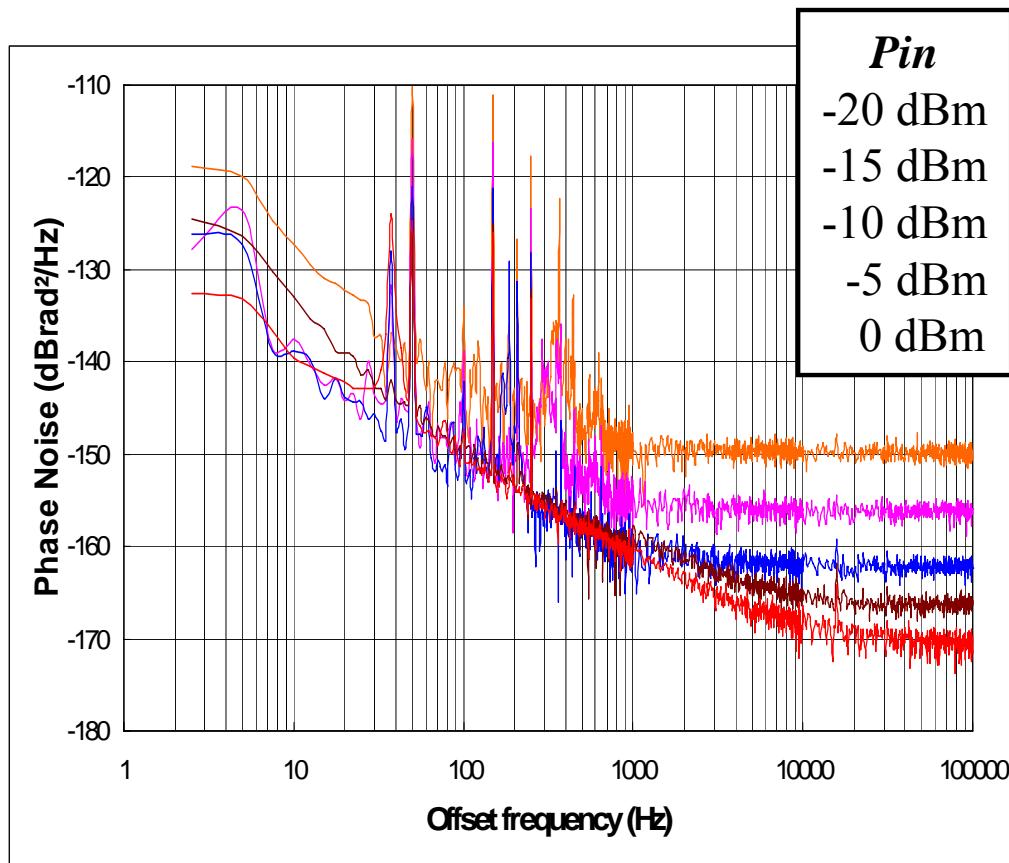
## Phase noise in microwave SiGe HBTs :

*Investigations on the phase noise of SiGe HBTs versus the transistor microwave input power*



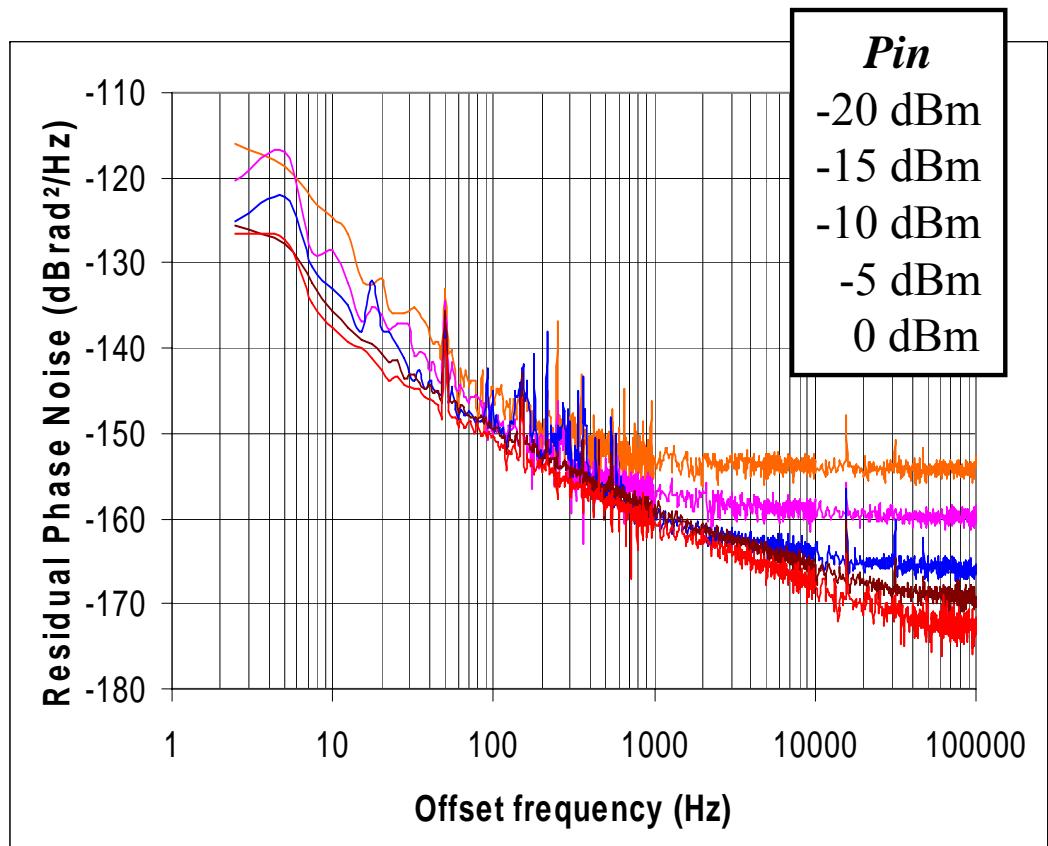*Case of SiGe HBT (LPNT32)  
loaded onto 50 Ω at 3.5 GHz  
from linear regime up to 1dB compression*





*Case of SiGe HBT (BFP620)  
loaded onto 50 Ω at 3.5 GHz  
from linear regime up to 1dB compression*
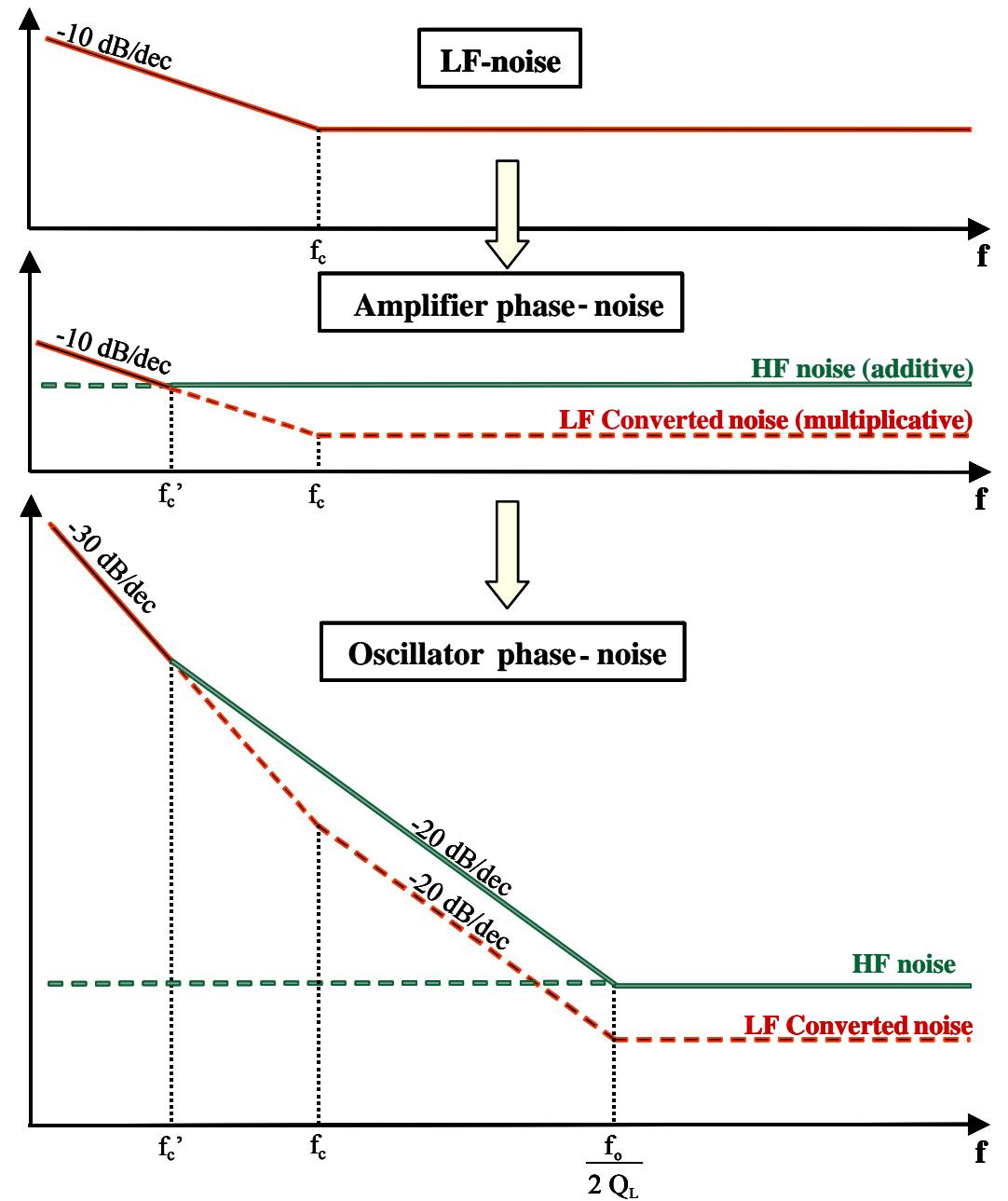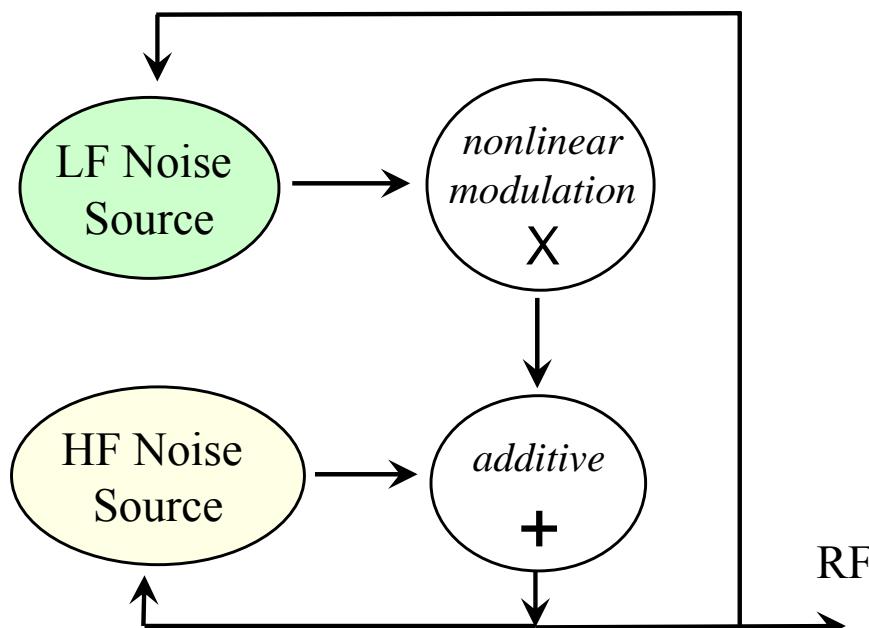
## Phase noise in microwave SiGe HBTs : discussion on the results versus $P_{in}$



*1/f phase noise is necessarily a conversion noise, and is related to the device LF noise*

*White phase noise can result either from a conversion process or be an additive noise*



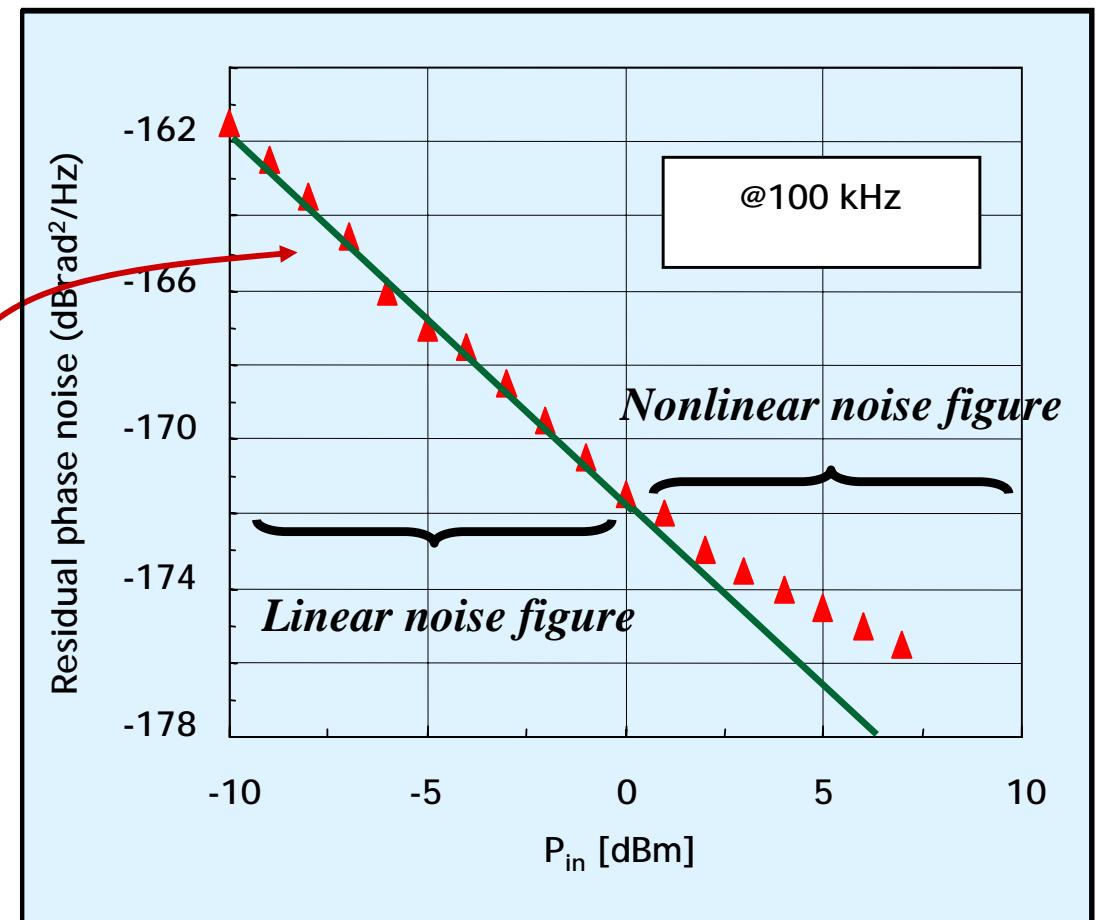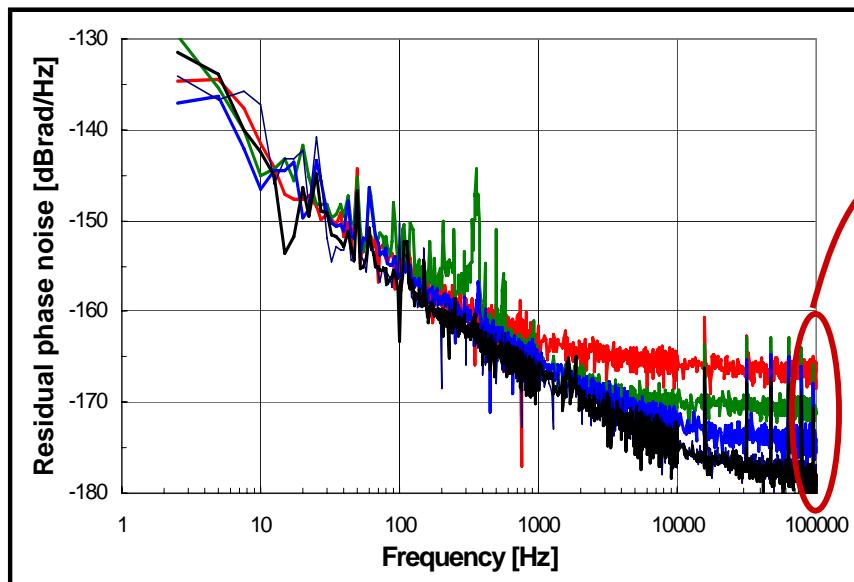
# Phase noise in microwave SiGe HBTs :

*phase noise floor analysis -> HF noise contribution to the phase noise*



*Signature of an additive phase noise*
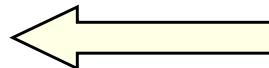
$$S_{\Phi add} = \frac{F_{dut} k T_0}{P_{in}}$$



*1 dB/dB slope, at least when the device is not too much driven into compression*


Cibiel et al., IEEE Trans. on MTT, jan. 2004

## Phase noise in microwave SiGe HBTs : *LF noise into phase noise conversion (modulation noise)*
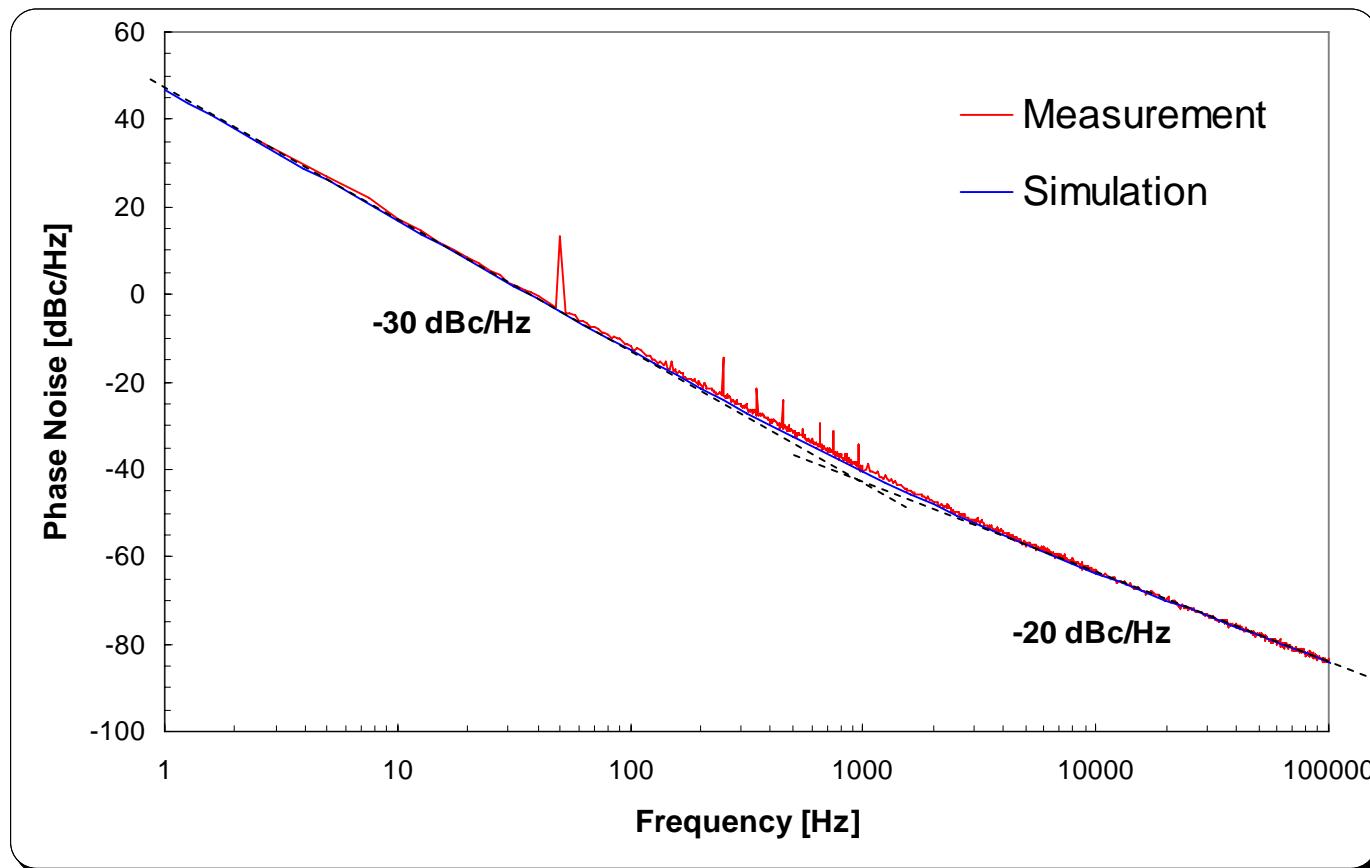
### 1) Case n° 1 : no special filtering of the Si<sub>be</sub> source


$$S_{i_{be}} = K \frac{I_{be_{DC}}^{\alpha}}{f^{\beta}} + 2q I_{be_{DC}}$$

The influence of this noise source is predominant. The phase noise is easy to calculate, but it is also about 15 dB higher than when this noise source effect is cancelled.



Ex : 10 GHz SiGe HBT VCO

Output

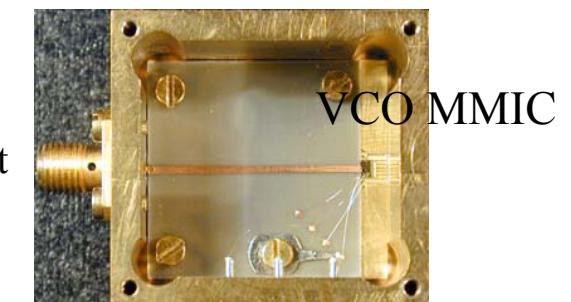




K. W. Wong et al., 2003 IEEE RFIC

# Phase noise in microwave SiGe HBTs : *LF noise into phase noise conversion (modulation noise)*


2) Case 2 : cancellation of  $S_{i_{be}}$  and extraction of the equivalent external  $S_{v_{be}}$  noise source with different microwave power applied on the device
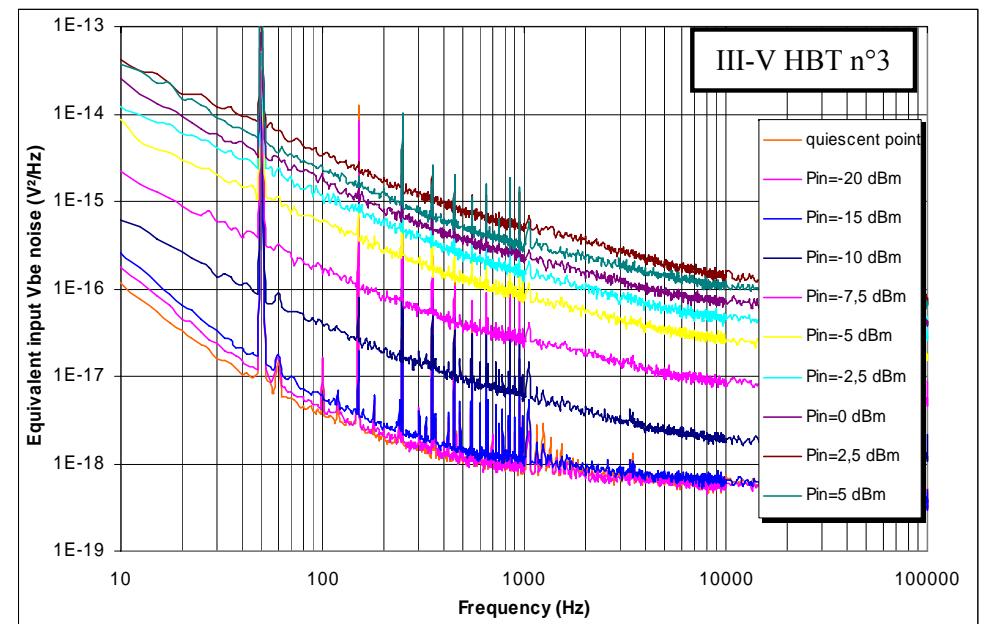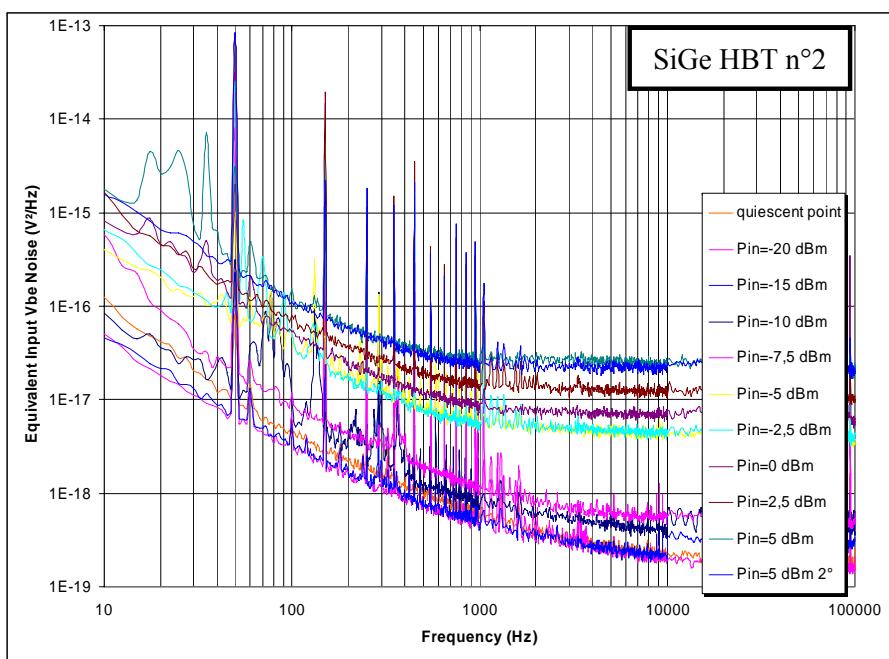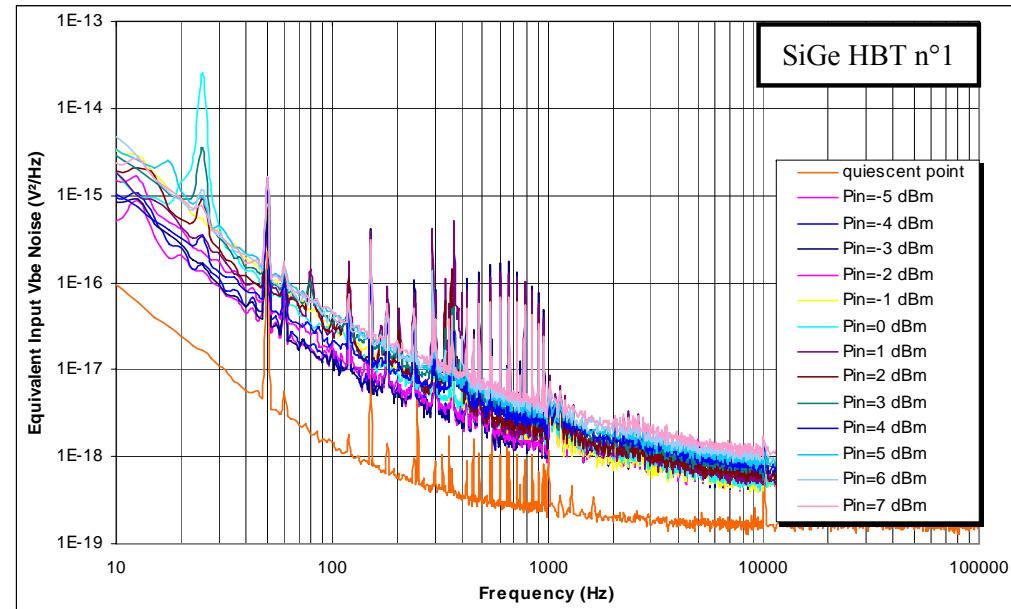
## Main difficulty :

The LF noise is modified by the large signal operation, and the amplitude of the change is very dependent on the device


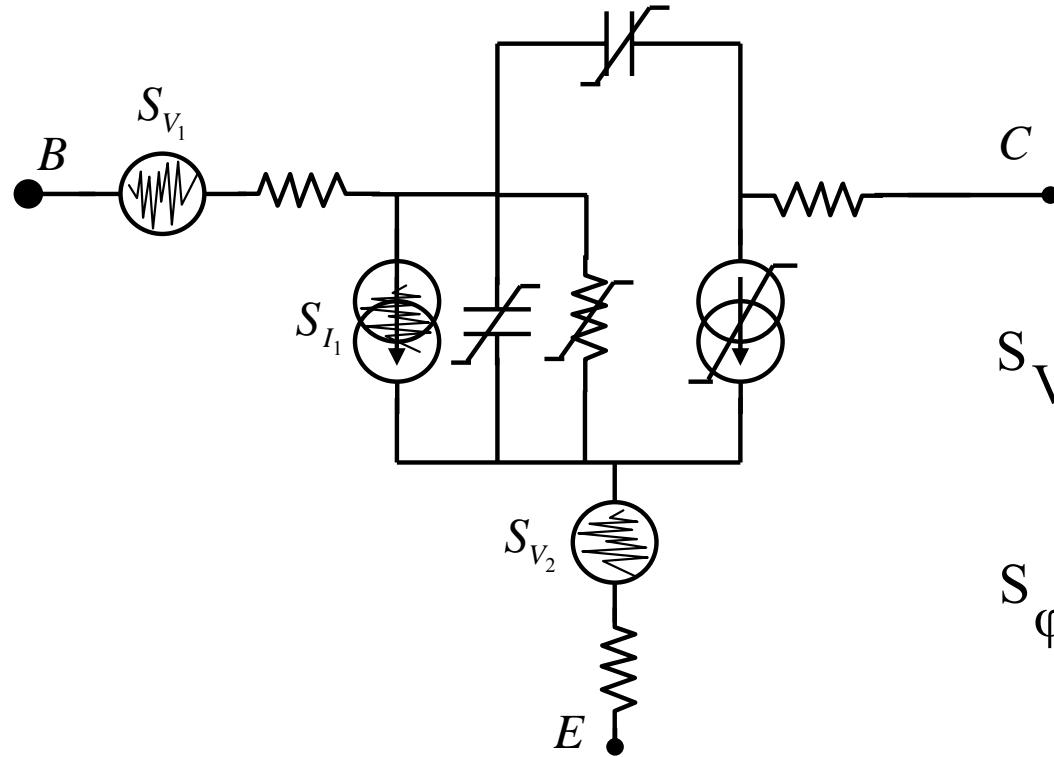
## Phase noise in microwave SiGe HBTs : *LF noise into phase noise conversion (modulation noise)*



$$S_{V_e} = \sum K_{BF}^2(V_{be}, V_{ce}) * S_i \text{ or } v$$


$$S_\phi = \sum K_\phi^2(V_{be}, V_{ce}) * S_i \text{ or } v$$

The LF noise sources location with respect to the device nonlinearities is essential to correctly compute the transfer functions  $K_{BF}$  and  $K_\phi$




However, according to recent studies on cyclostationary noise, this noise description may not be sufficient and it may be necessary to take into account the nonlinear behaviour at the noise source level

## Approach using nonlinear noise sources

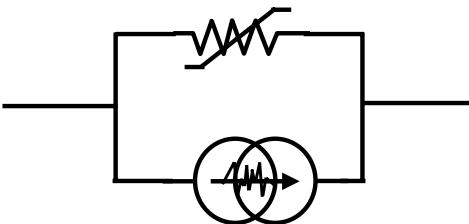Example : implementation of a nonlinear voltage noise source




or ?

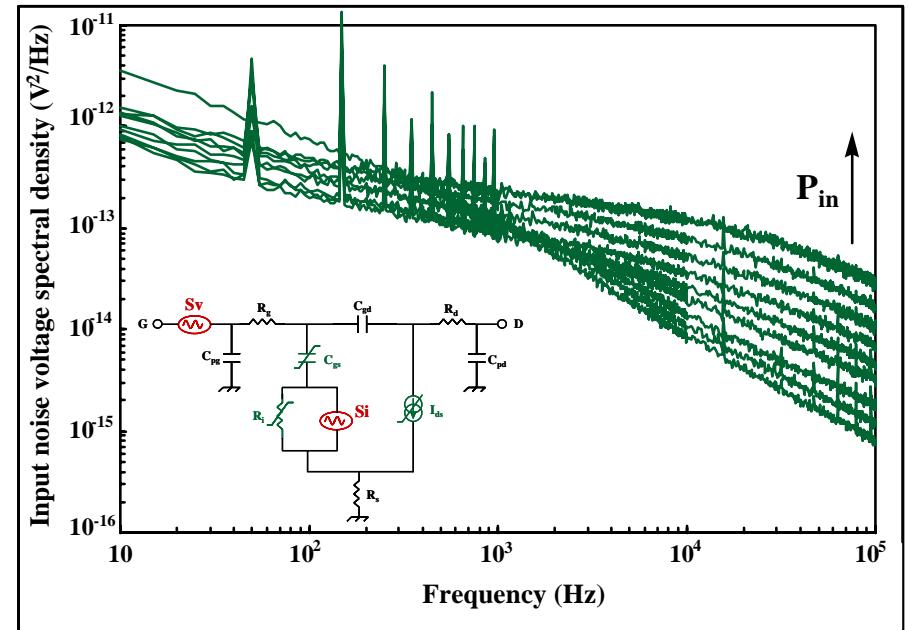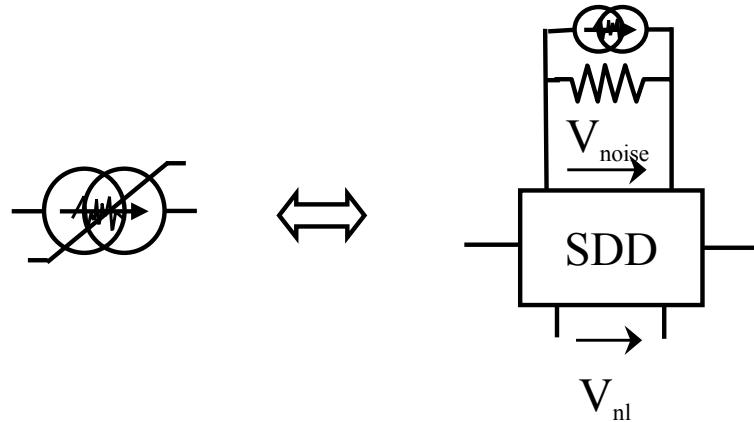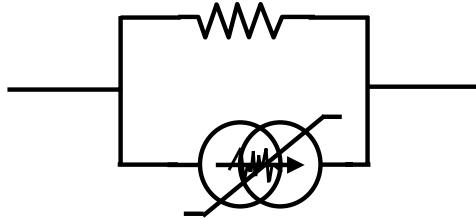


*Example of a model developed for a HEMT device, including a current noise source associated to a non-linear resistance, to generate a nonlinear LF noise voltage equivalent behavior*

*O. Llopis et al., 2001 IEEE MTT S.*
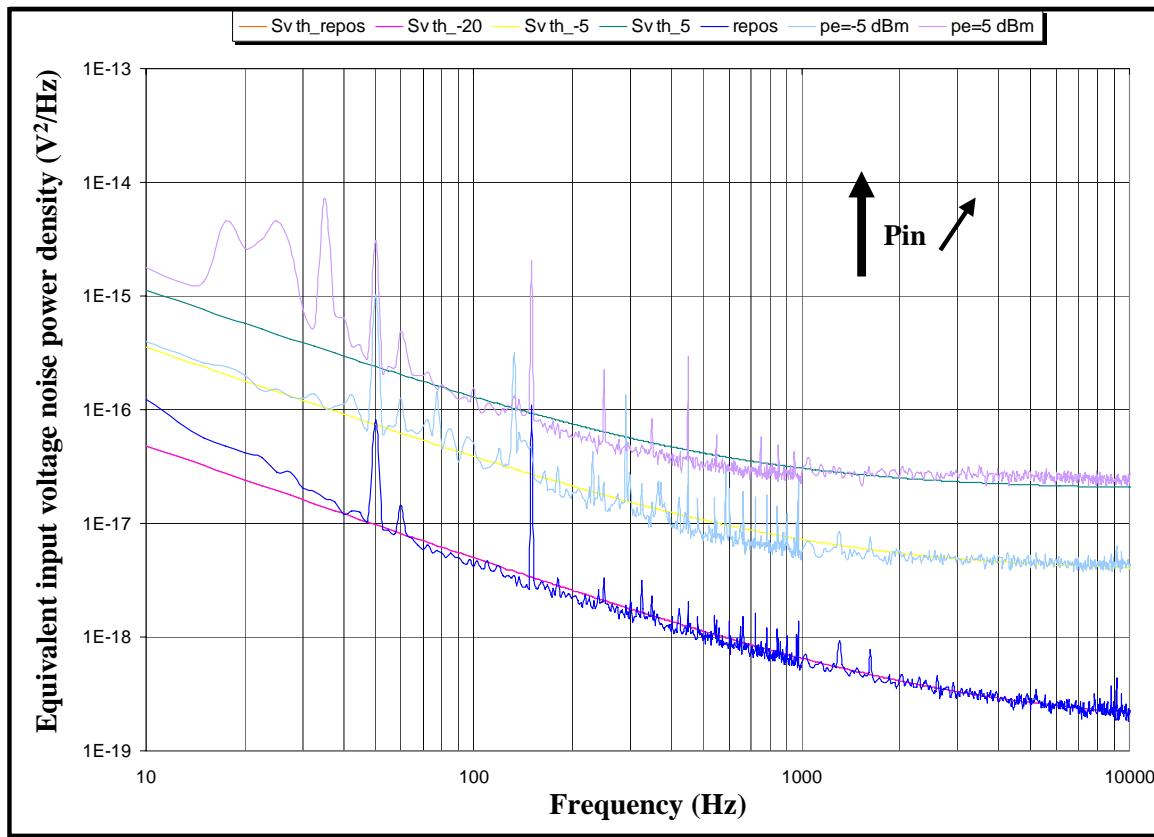
## Alternative approach : a RF power dependent external voltage noise source



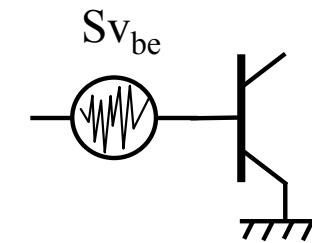*Equivalent input voltage noise of an SiGe HBT (BFP620)  
submitted to a 3.5 GHz large signal, from linear regime up  
to 1 dB compression (RF load = 50  $\Omega$ )*



Model obtained with two empirical factors :

$$k_1 = a_1 * \left( e^{-\frac{P_{in}}{b_1}} - \frac{1}{c_1} \right)$$

$$k_2 = a_2 * \left( e^{-\frac{P_{in}}{b_2}} - \frac{1}{c_2} \right)$$

$$S_{v_{be}}(P_{in}) = \left( S_{v_{1/f}} + k_1(P_{in}) * S_{v_{floor}} \right) * \left( 1 + k_2(P_{in}) \right)$$

Gribaldo et al., 2005 ICNF

## Phase noise in microwave SiGe HBTs : simulating the overall amplifier phase noise

### Harmonic Balance

LF noise conversion




sensitivity techniques

or pnmx

HF noise addition (nonlinear)




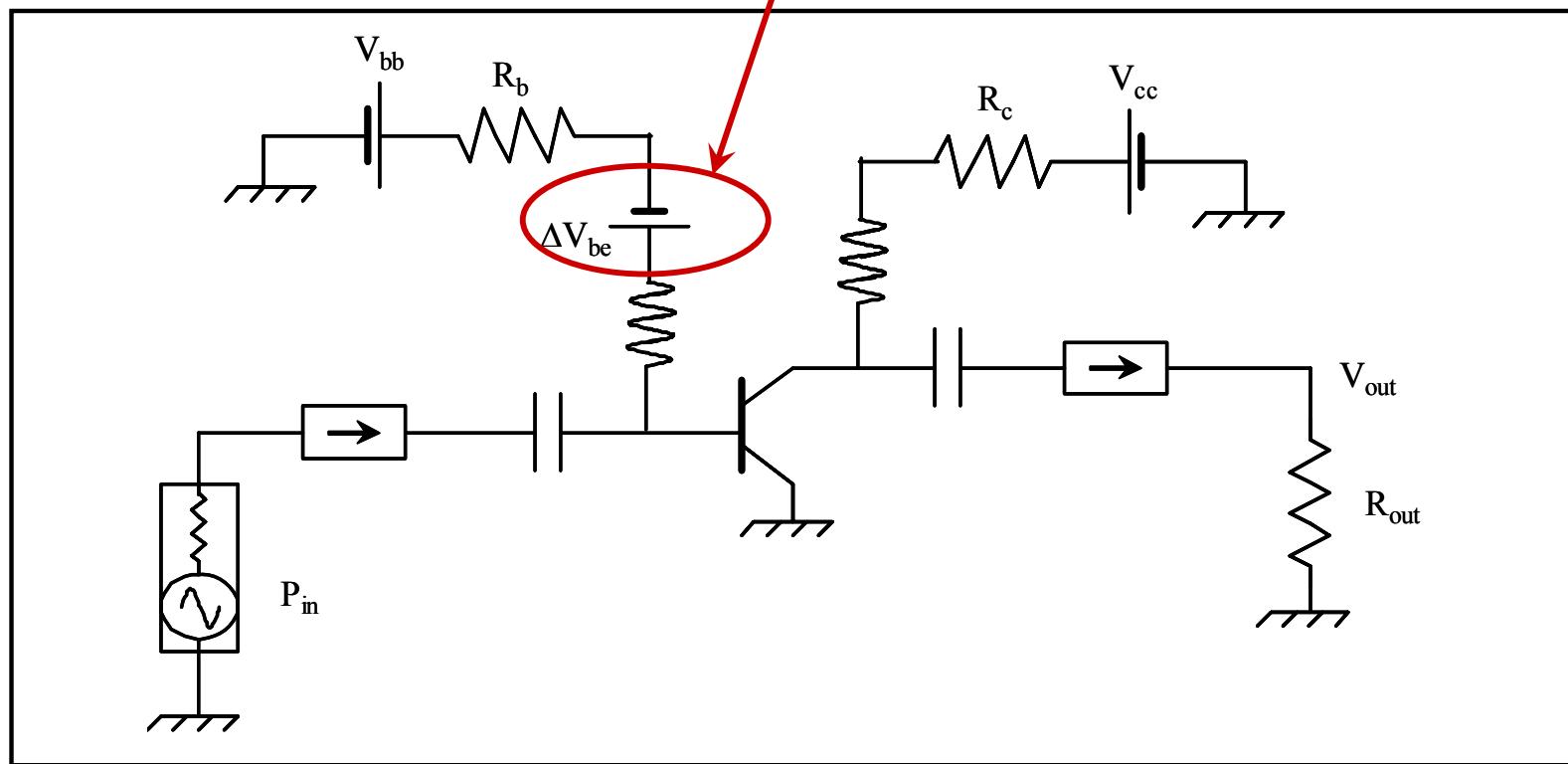
analytical using  $F_{\text{nonlinear}}$  or pnmx



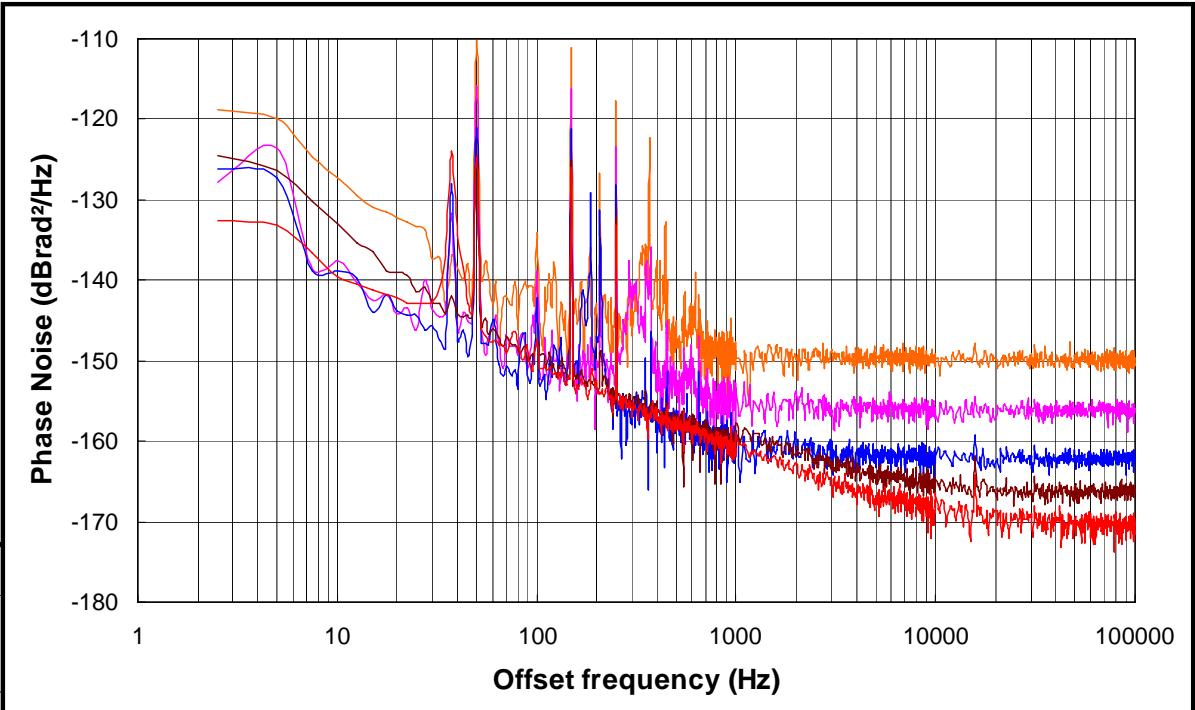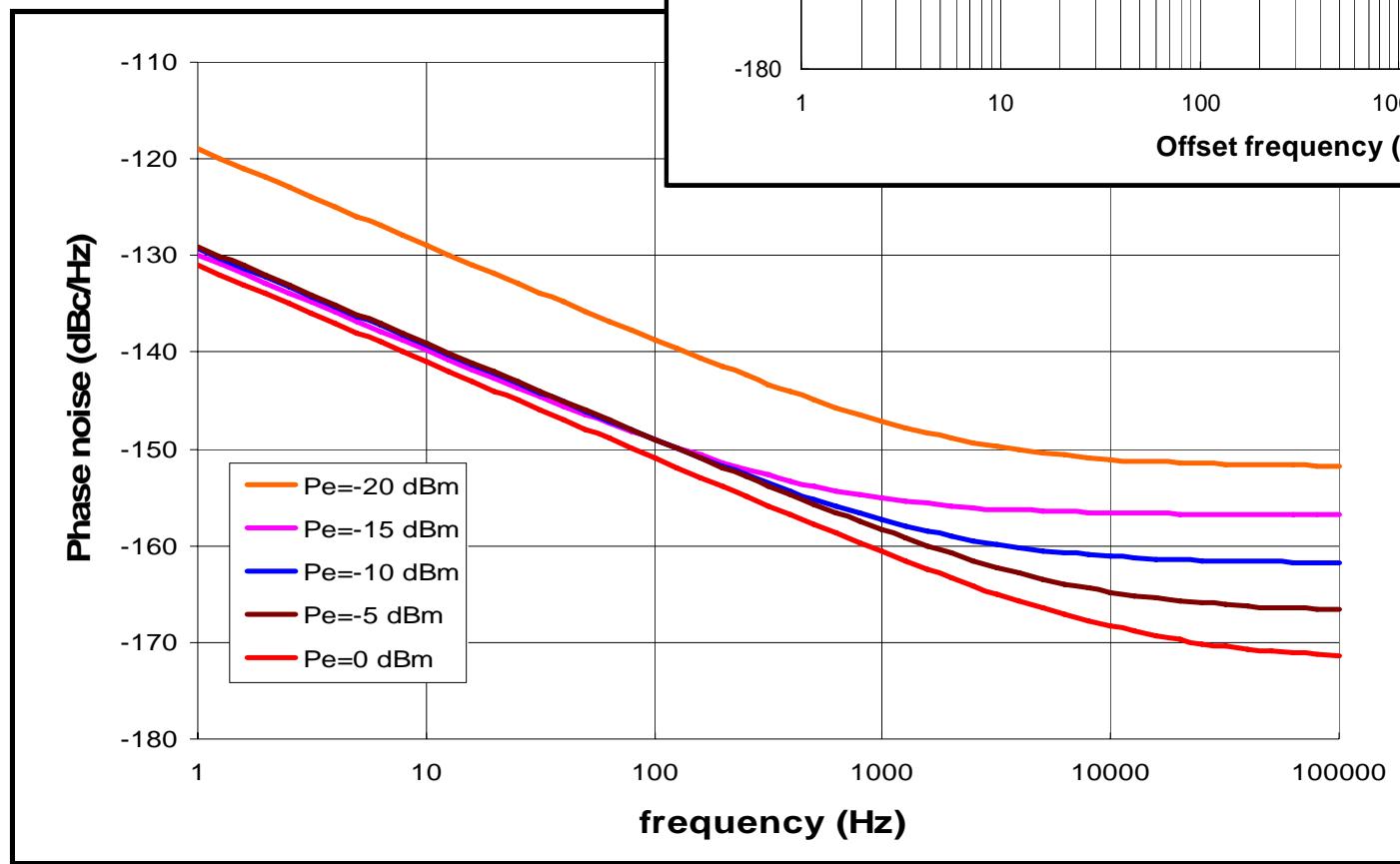
## Simulation / measurement

SiGe HBT loaded onto  $50 \Omega$   
at 3.5 GHz

from linear regime  
to small compression



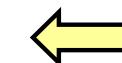Gummel-poon HBT  
model, using an extrinsic  
LF noise source  
dependent on the  
microwave RF power



S. Gribaldo et al., 2005 ICNF

## Phase noise optimisation

### 1) Case of an hybrid DRO (or any resonator stabilised oscillator)

**High quality Oscillator** = **low phase noise amplifier** + **high loaded Q resonator**

**Resonator :** Coupling factor involving at least 4 dB losses

**Amplifier :** Transistors selection using residual phase noise data

LF loading circuitry (bias network)

Close to the carrier phase noise (multiplicative)

- minimisation of the LF noise conversion varying the transistor RF loads and the circuit topology (using CAD)

Far from carrier phase noise (additive)

- minimisation of the transistor nonlinear noise figure (using CAD)
- optimum resonator coupling close to 6 dB

### 2) Case of an integrated VCO (MMIC)

LF loading circuitry (bias network)

- more difficult, because of the required size of the decoupling inductors

Optimisation of circuit topology (and transistor RF load) using a fast enough computing approach (ex : sensitivity technique)

# Phase noise optimisation

## 3) Problem of gain & phase noise trade-off

### 3.1) Additive phase noise :

*Amplifier :*


$$S_\phi = \frac{F k T G}{P_{sat}}$$

$S_\phi \uparrow$  when  $G \uparrow$

*Resonator :*

$Q_L \uparrow$  when  $L \uparrow$

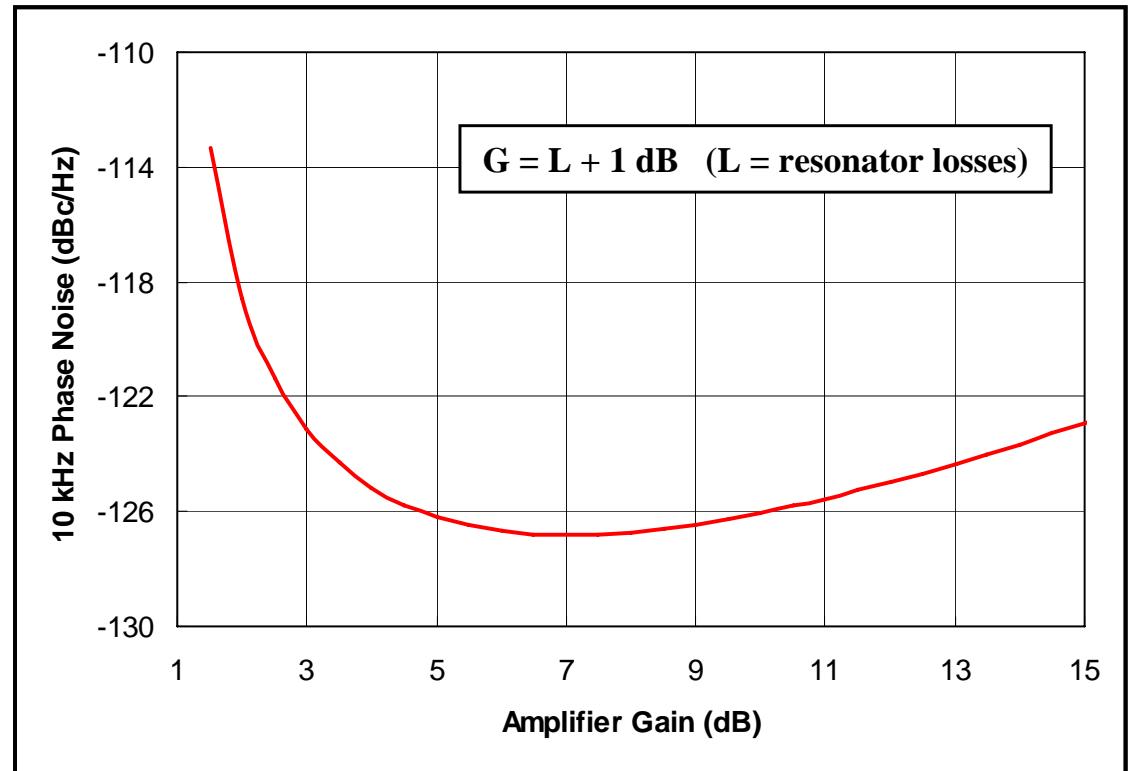➡ **Optimum gain  $G$ , or coupling losses  $L$**



*Oscillator phase noise versus amplifier gain, with a constant Noise Figure and at 1 dB compression ( $f_o = 10$  GHz,  $Q_o = 10^4$ )*


$$L(f_m) \text{ in } \text{dBc/Hz} = 20 \log \left( \frac{\frac{f_0}{2\sqrt{2} f_m Q_o}}{\frac{10^{\frac{G_o-1}{20}}}{10^{\frac{G_o-1}{20}} - 1}} \right) + 10 \log \left( \frac{F k T_o}{P_{sat}} \right) + G_o$$

# Phase noise optimisation

## 3) Problem of gain & phase noise trade-off
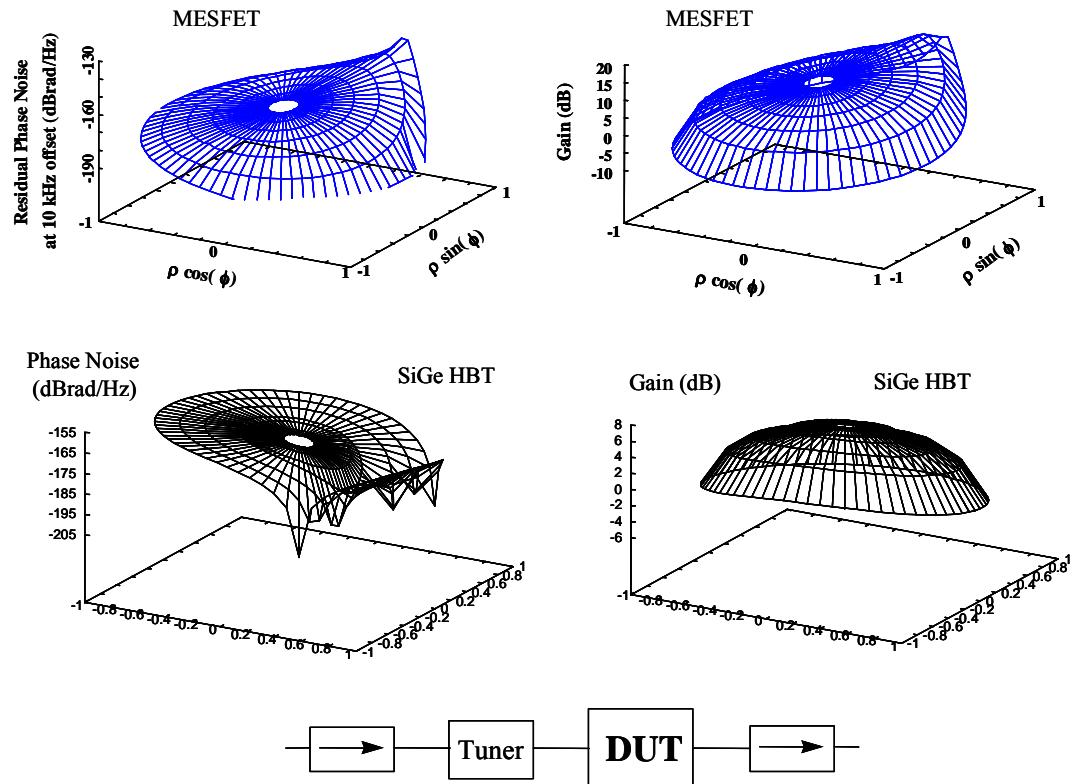
### 3.2) Conversion phase noise :

*Gain matching, particularly at the transistor input, increases the LF noise conversion because of the resonant behaviour of the input nonlinear capacitance*



Juraver et al., 2000 EuMC (FET)

Régis et al., IEEE Trans. on MTT, oct. 1998 (Bipolar)



*It is almost impossible to get, with a one stage amplifier, both high gain and low phase noise  
Equivalently, it is very difficult to reach low phase noise close to the device cut-off frequency*


## Problem of gain & phase noise : two stages amplifier solution

Theory :

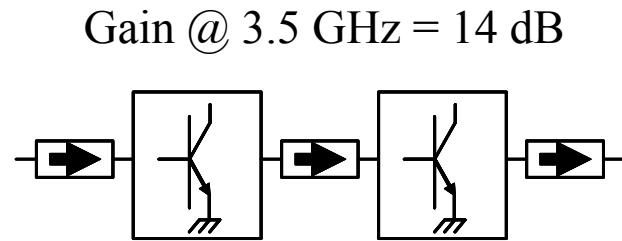- 1) Conversion noise (1/f noise) is added :  $\overline{\Delta\phi_{\text{two stages}}^2} = \overline{\Delta\phi_{\text{1st stage}}^2} + \overline{\Delta\phi_{\text{2nd stage}}^2}$   
→ 3 dB increase of the 1/f noise  
in case of two stages working in the same conditions
- 2) Additive noise is dominated by the first stage noise


1rst experiment :

Two identical SiGe HBTs between  $50\Omega$  isolators



Comparison between phase noise of one stage and two stages amplifier, with identical devices and at the same input power (0 dBm) →

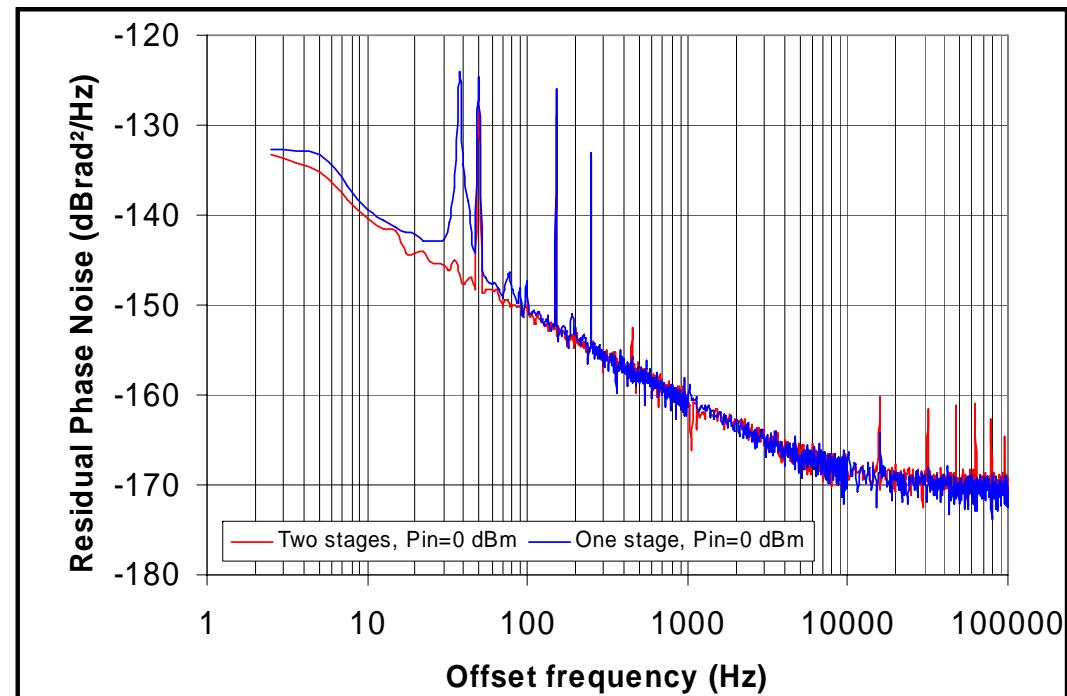*In this case : phase noise is dominated by the first stage amplifier, both for the 1/f noise or additive noise contributions*




## Problem of gain & phase noise : two stages amplifier solution

Prototype of a two stage amplifier for a 9.6 GHz application

SiGe HBT + Si BJT

8.2 dB Power Gain

-163 dBrad<sup>2</sup>/Hz @ 10 kHz

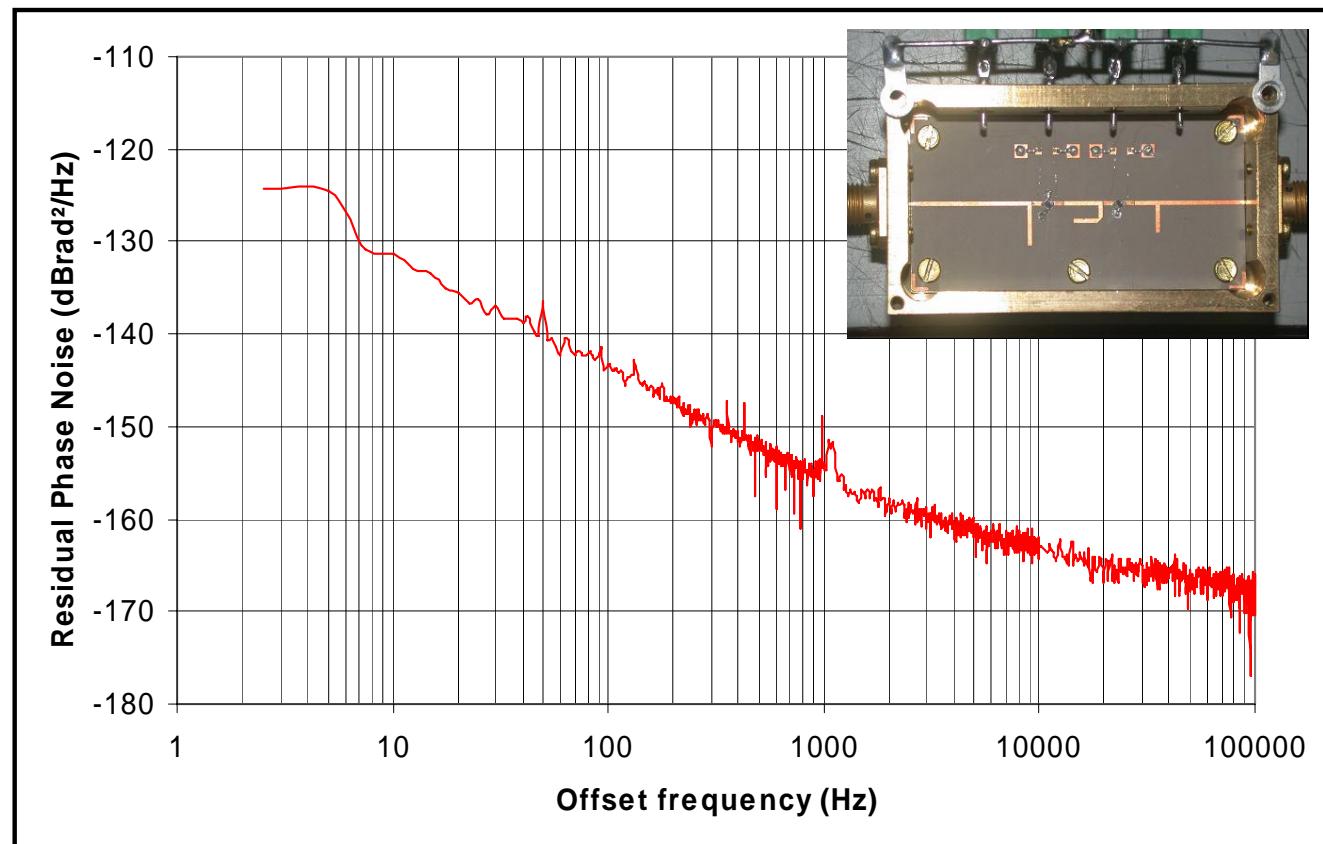

$$L(f_m)_{\text{in } \text{dBc/Hz}} = 20 \log \left( \frac{f_0}{2\sqrt{2} f_m Q_0} \frac{\frac{L}{10^{20}}}{10^{\frac{L}{20}} - 1} \right) + S_{\Phi}^{\text{amplifier in } \text{dBrad}^2 / \text{Hz}}$$

$$Q_0 = 2 \cdot 10^5 \quad L = 6 \text{ dB}$$


Application :

Ultra low phase noise X band sapphire oscillator

**-152 dBc/Hz @ 10 kHz offset predicted**

S. Gribaldo et al. 2005 EFTF and IEEE Freq. Control Symp
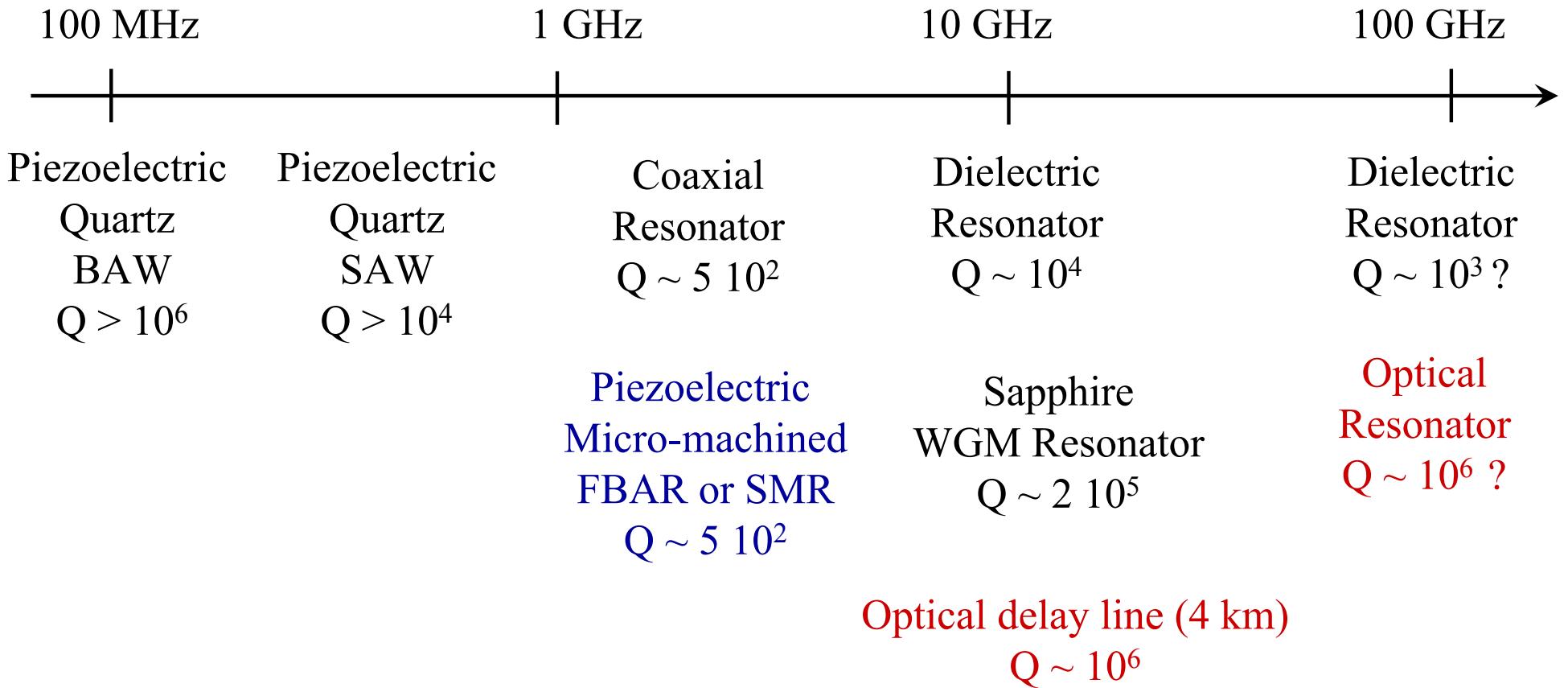
## The evolution of HF resonators for oscillator stabilisation




*Question : what about noise and phase noise in these new devices ?  
(piezoelectric or optic devices)*


# Phase noise in resonators : micro-machined piezoelectric resonators

## Investigating the frequency and phase fluctuations of FBAR resonators for MMIC applications


FBAR = Film Bulk Acoustic Resonator

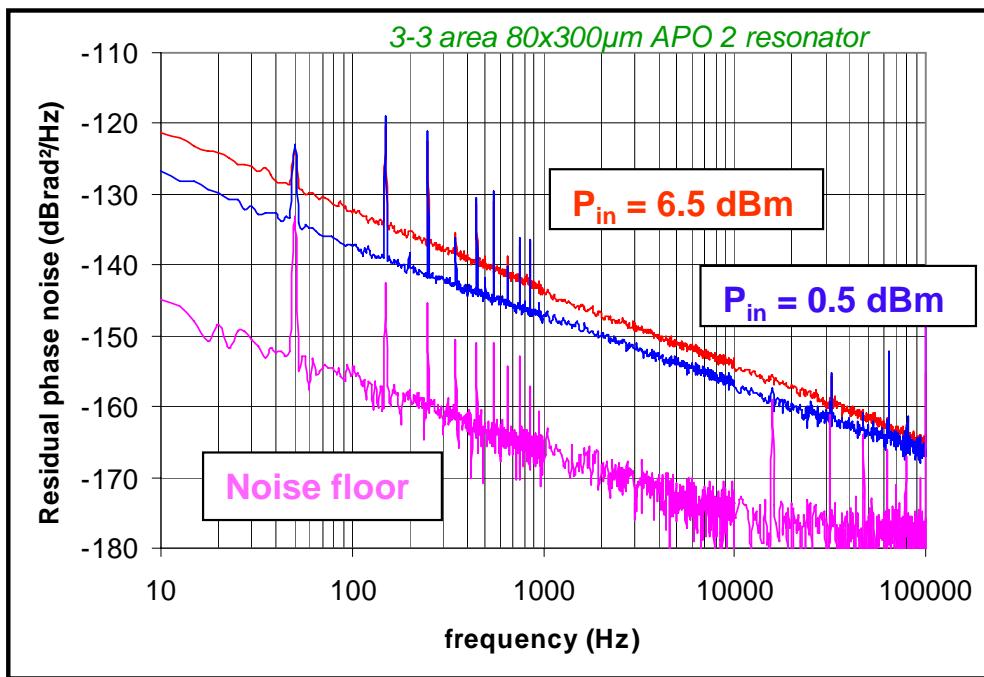

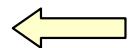
Evidence of a RF power dependent ( $\leftrightarrow$  nonlinear) close to 1/f phase fluctuation through the resonator



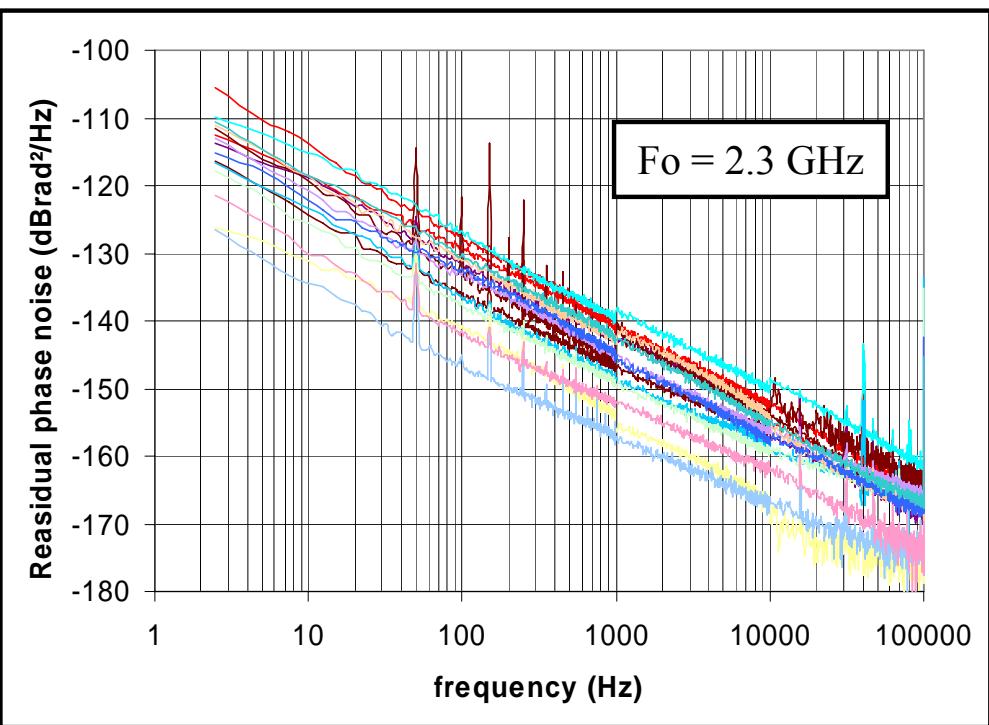This 1/f phase fluctuation of the signal is caused by a 1/f fluctuation of the resonator center frequency



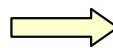Phase noise measurement, using a probe test set, of 14 resonators with different geometries integrated above IC on Silicon substrate






Evidence of a large dispersion of the results

## Phase noise in resonators : *micro-machined piezoelectric resonators*
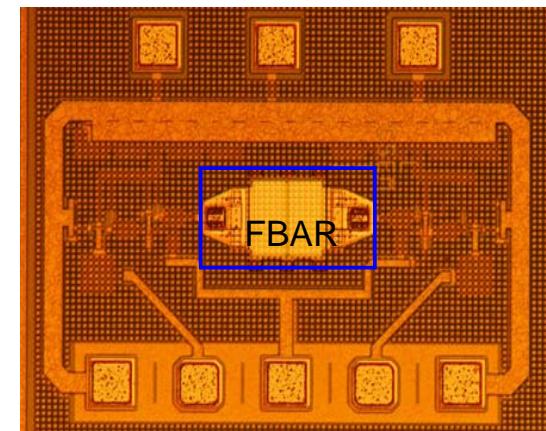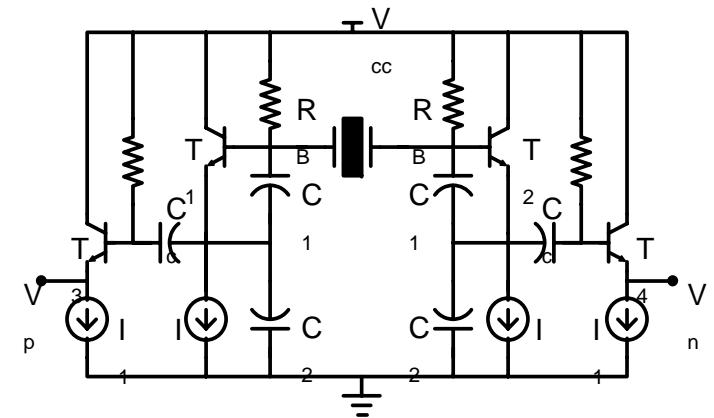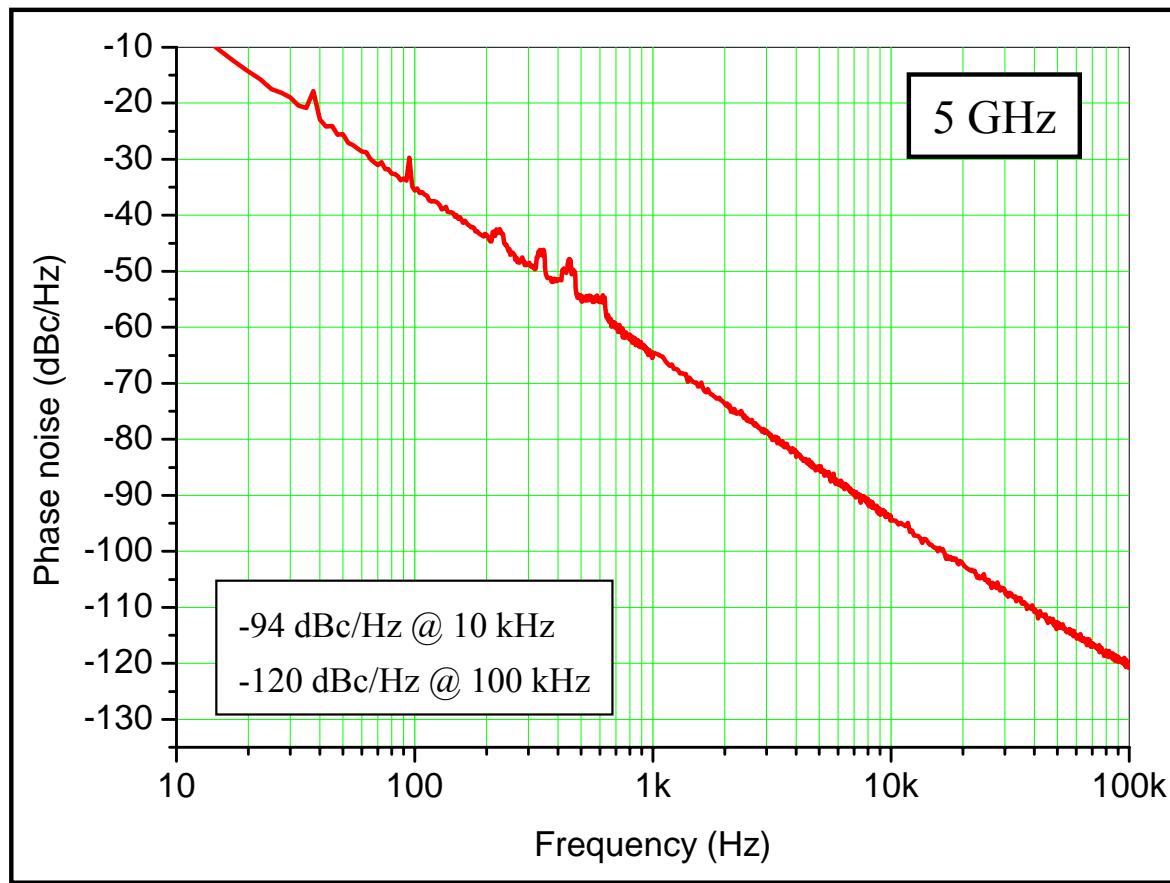
### Phase noise measurement of an integrated 5 GHz FBAR oscillator



→ evidence of the main influence of the resonator 1/f noise



M. Aissi et al., 2006 IEEE ISSCC

## Phase noise in resonators : *optical devices for microwave applications*

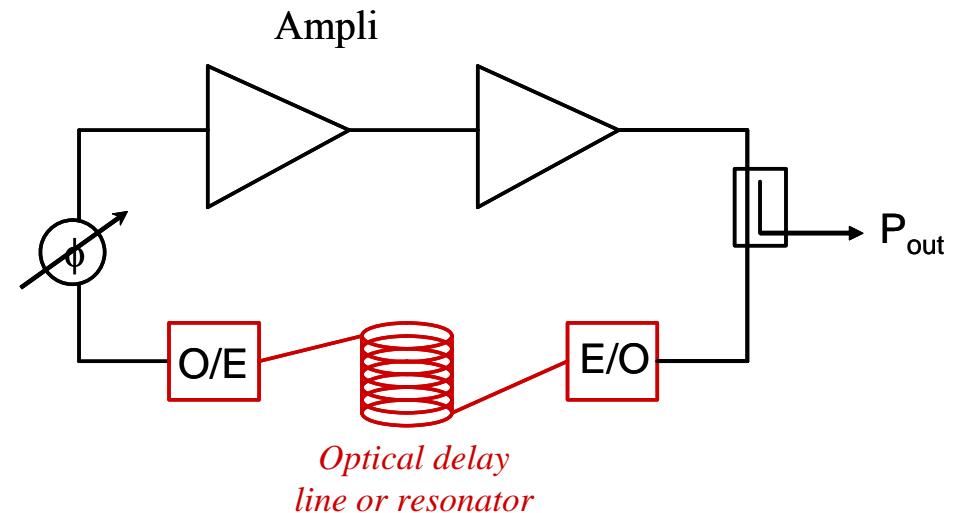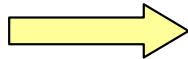Example of an optical-microwave oscillator



In these applications, the phase noise comes both from the RF amplifiers and from the optical to microwave or microwave to optical conversions - it may also be generated in long fiber optics delay lines (above  $\sim 5$  km)

Optical to microwave  $\longrightarrow$  laser noise (RIN)

Microwave to optical  $\longrightarrow$  photodiode noise

# Phase noise in resonators : *optical devices for microwave applications*

## Example :


Phase noise of different optical links at microwave frequencies  
(output at X band)

### *1) Noise floor*

well predicted with analytical equations

### *2) "1/f" contribution*

surprisingly low

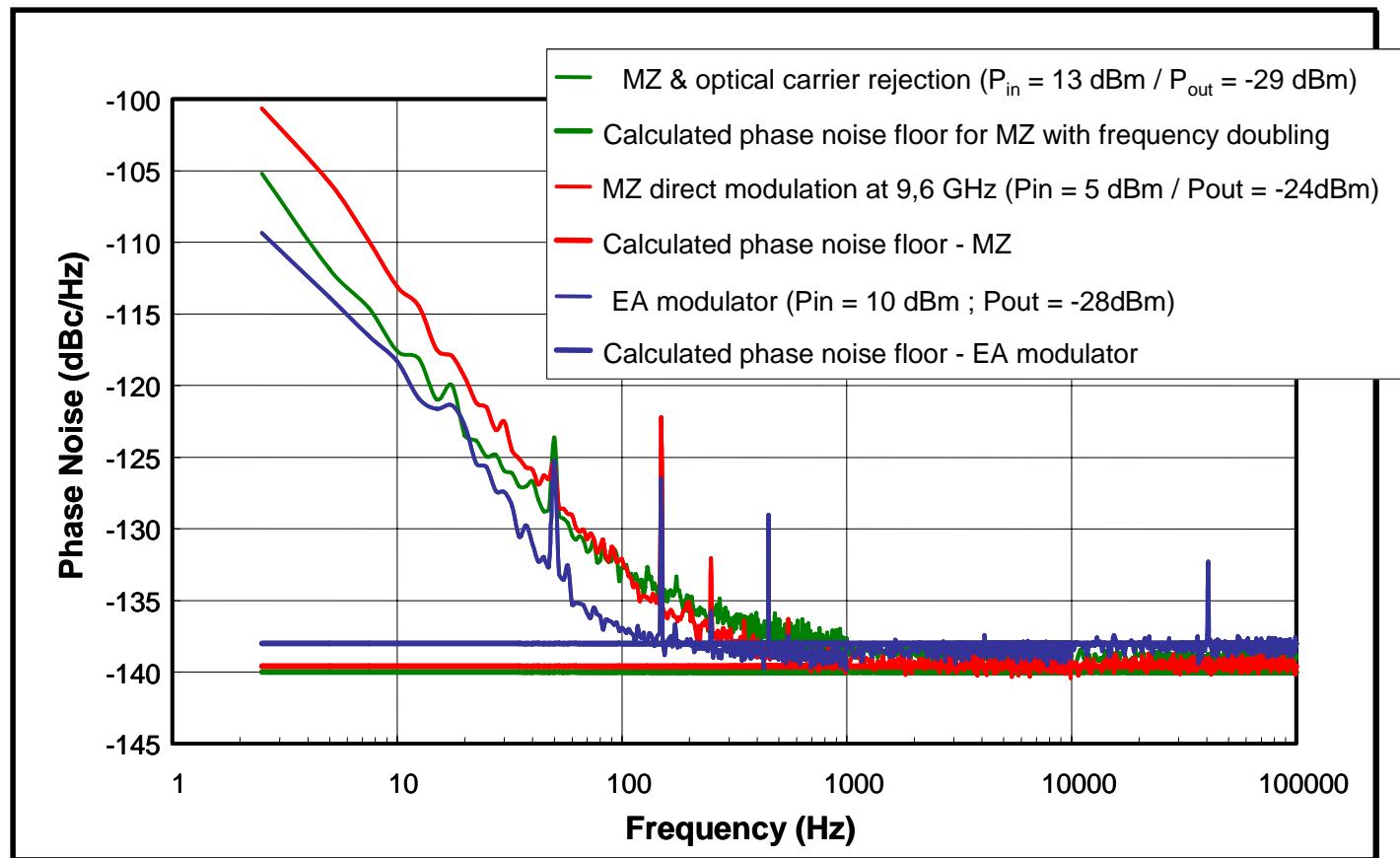


## Analytical modeling :

$$CNR = \frac{P_{\text{det}}^2 \cdot S^2 \cdot m^2}{2 \cdot (P_{\text{det}}^2 \cdot S^2 \cdot RIN + 2 \cdot q \cdot (S \cdot P_{\text{det}} + i_{\text{obs}}))}$$

$$S_{\phi \text{ input}} = K \cdot \frac{RIN_{LF_0}}{f_m} + \frac{1}{(2 \cdot CNR)}$$

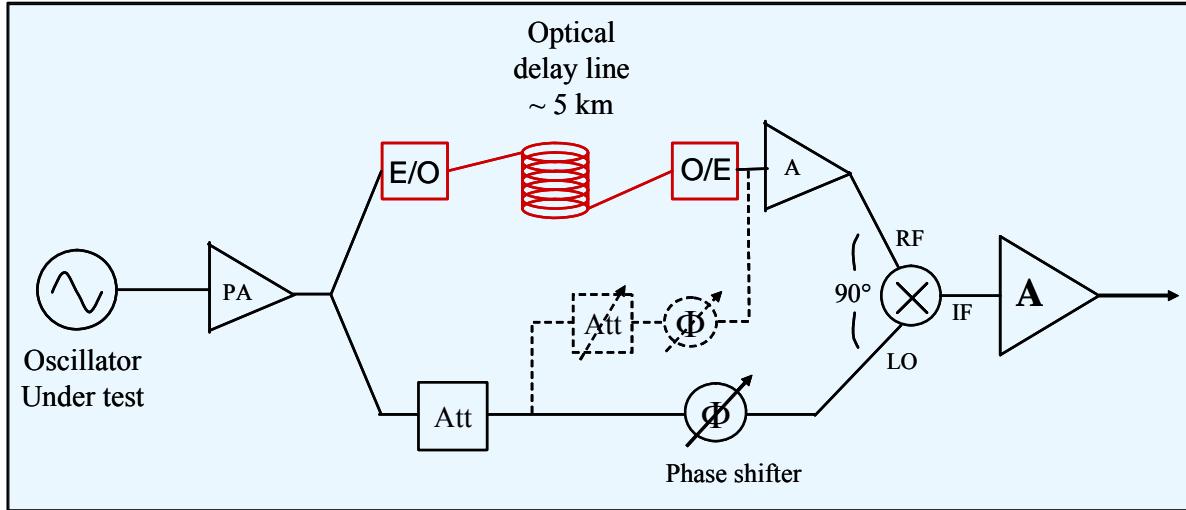B. Onillon et al. 2005 IEEE Freq. Control Symp



## Application example :

Ultra high sensitivity  
delay line microwave  
frequency discriminator


### Possible use :

Phase noise metrology

Radar

May be telecommunications  
if the delay can be integrated  
(resonator instead of a delay  
line)

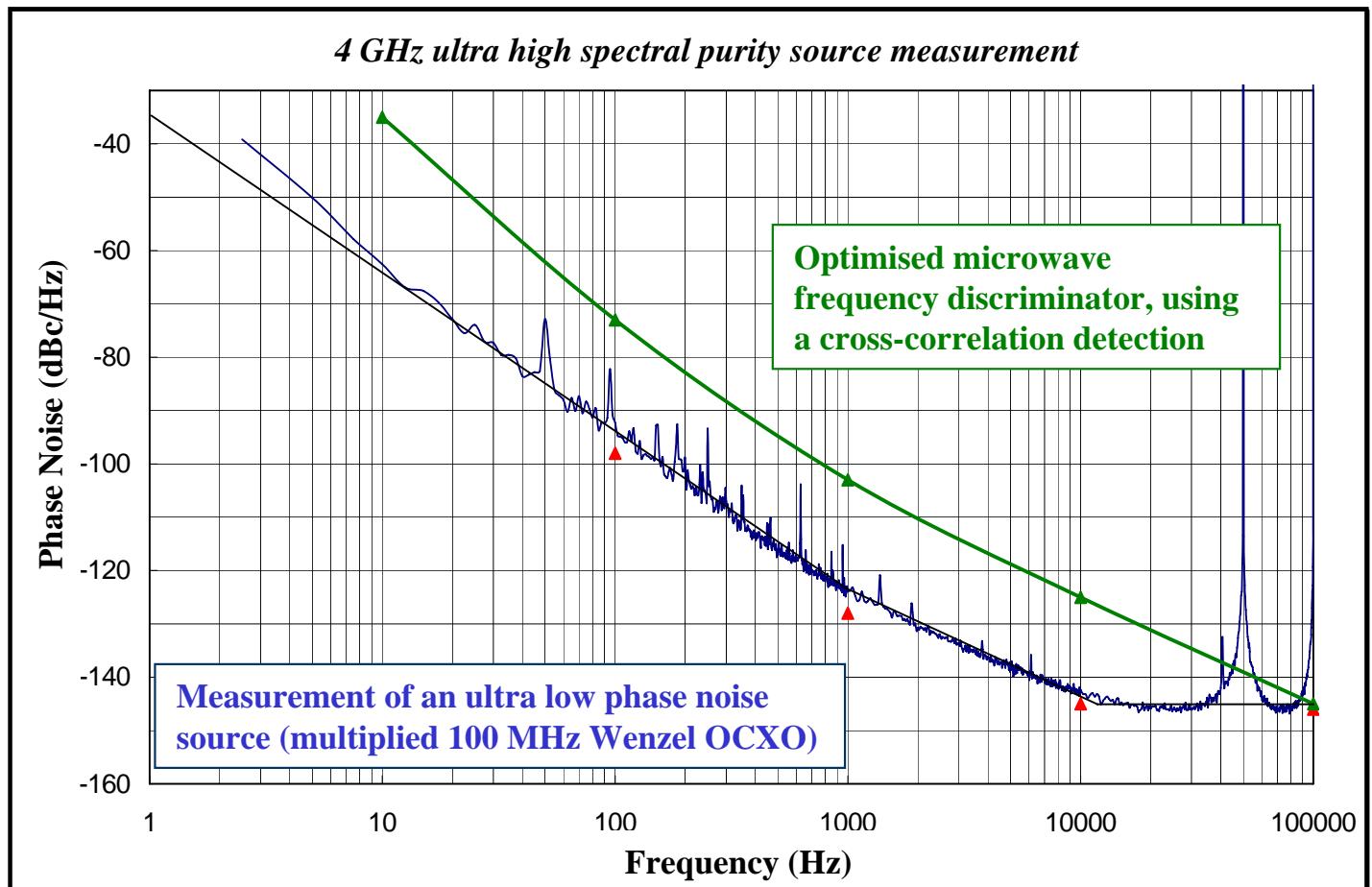B. Onillon et al., 2005  
IEEE Int. Freq. Control Symp.



# Conclusion

## Residual phase noise measurement

⇒ *An efficient tool for fundamental investigations on nonlinear noise*

## Amplifier phase noise modelling – the problem of conversion noise

⇒ *Nonlinear noise source or external RF power dependent noise source*

## Gain and phase noise trade-off

⇒ *Investigations on two stages amplifiers*

## Phase noise in new devices for frequency stabilization at microwave frequencies (piezoelectric or optical resonators)

⇒ *A new field of investigation*